



## *EE141-Fall 2012 Digital Integrated Circuits*

### Lecture 11 MOS Capacitance and Delay

## *Announcements*

- No labs this week
  - Labs restart next week
  
- Midterm #1 Thurs. Oct. 4<sup>th</sup>, 6:30-8:00pm
  - Exam is open notes, book, calculators, etc.
  - Covers up to lecture 10


## *Class Material*

- Last lecture
  - Using the MOS model: Inverter VTC
- Today's lecture
  - MOS Capacitance
  - Using the MOS Model: Delay
- Reading (3.3.2, 5.4.2)

## *MOS Capacitance*



## MOS Capacitances

 

EECS141

Lecture #11

5

## Gate Capacitance

- Capacitance (per area) from gate across the oxide is  $W \cdot L \cdot C_{OX}$ , where  $C_{OX} = \epsilon_{OX} / t_{OX}$ 
  - But channel isn't really a terminal in my MOS transistor model...

EECS141


Lecture #11

6

## Gate Capacitance


- Distribution between terminals is complex
  - Capacitance is really distributed
    - Useful models lump it to the terminals
  - Several operating regions:
    - Way off, off, transistor linear, transistor saturated

## Transistor In Cutoff

 

- When the transistor is off, no carriers in channel to form the other side of the capacitor.
  - Substrate acts as the other capacitor terminal
  - Capacitance becomes series combination of gate oxide and depletion capacitance

## Transistor In Cutoff (cont'd)

 


- When  $|V_{GS}| < |V_T|$ , total  $C_{GCB}$  much smaller than  $W \cdot L \cdot C_{ox}$ 
  - Usually just approximate with  $C_{GCB} = 0$  in this region.
- (If  $V_{GS}$  is “very” negative (for NMOS), depletion region shrinks and  $C_{GCB}$  goes back to  $\sim W \cdot L \cdot C_{ox}$ )

EECS141

Lecture #11

9

## Transistor in Linear Region

 


- Channel is formed and acts as the other terminal
  - $C_{GCB}$  drops to zero (shielded by channel)
- Model by splitting oxide cap equally between source and drain
  - Changing either voltage changes the channel charge

EECS141

Lecture #11


10

## Transistor in Saturation Region

 


- Changing source voltage doesn't change  $V_{GC}$  uniformly
  - E.g.  $V_{GC}$  at pinch off point still  $V_{TH}$
- Bottom line:  $C_{GCS} \approx 2/3 \cdot W \cdot L \cdot C_{ox}$
 
## Transistor in Saturation Region (cont'd)




- Drain voltage no longer affects channel charge
  - Set by source and  $V_{DS\_sat}$
- If change in charge is 0,  $C_{GCD} = 0$

## Gate Capacitance


 


 $C_{gate}$  vs.  $V_{GS}$   
(with  $V_{DS} = 0$ )



$C_{gate}$  vs. operating region


## Gate Overlap Capacitance

  

$$C_O = C_{ox} \cdot x_d$$

Off/Lin/Sat  $\rightarrow C_{GSO} = C_{GDO} = C_O \cdot W$

## Gate Fringe Capacitance

 

- $C_{OV}$  not just from metallurgic overlap – get fringing fields too
- Typical value:  $\sim 0.2\text{fF}\cdot W(\text{in } \mu\text{m})/\text{edge}$


EECS141

Lecture #11

15

## Diffusion Capacitance

- Bottom
  - Area cap
  - $C_{\text{bottom}} = C_j \cdot L_S \cdot W$
- Sidewalls
  - Perimeter cap
  - $C_{\text{sw}} = C_{j\text{sw}} \cdot (2L_S + W)$
- GateEdge
  - $C_{\text{ge}} = C_{j\text{gate}} \cdot W$
  - Usually automatically included in the SPICE model

 

EECS141

Lecture #11

16



## Junction Capacitance (2)


- Junction caps are nonlinear

- $C_J$  is a function of junction bias

- SPICE model equations:

- Area  $C_J = \text{area} \times C_{J0} / (1 + |V_{DB}|/\phi_B)^{mj}$
  - Perimeter  $C_J = \text{perim} \times C_{JSW} / (1 + |V_{DB}|/\phi_B)^{mjsw}$
  - Gate edge  $C_J = W \times C_{Jgate} / (1 + |V_{DB}|/\phi_B)^{mjswg}$

 - How do we deal with nonlinear capacitance?



## Linearizing the Junction Capacitance

Replace non-linear capacitance by  
**large-signal equivalent linear capacitance**  
 which displaces equal charge over voltage swing of interest

$$C_{eq} = \frac{\Delta Q_j}{\Delta V_D} = \frac{Q_j(V_{high}) - Q_j(V_{low})}{V_{high} - V_{low}} = K_{eq} C_{j0}$$

$$K_{eq} = \frac{-\phi_0^m}{(V_{high} - V_{low})(1-m)} [(\phi_0 - V_{high})^{1-m} - (\phi_0 - V_{low})^{1-m}]$$

## Capacitance Model Summary

### □ Gate-Channel Capacitance

- $C_{GC} \approx 0$  ( $|V_{GS}| < |V_T|$ )
- $C_{GC} = C_{ox} \cdot W \cdot L_{eff}$  (Linear)
  - 50% G to S, 50% G to D
- $C_{GC} = (2/3) \cdot C_{ox} \cdot W \cdot L_{eff}$  (Saturation)
  - 100% G to S

### □ Gate Overlap Capacitance

- $C_{GSO} = C_{GDO} = C_O \cdot W$  (Always)

### □ Junction/Diffusion Capacitance

- $C_{diff} = C_j \cdot L_S \cdot W + C_{jsw} \cdot (2L_S + W) + C_{jg} W$  (Always)

EECS141

Lecture #11

19

## Capacitances in 0.25 $\mu\text{m}$ CMOS Process

	$C_{ox}$ (fF/ $\mu\text{m}^2$ )	$C_O$ (fF/ $\mu\text{m}$ )	$C_j$ (fF/ $\mu\text{m}^2$ )	$m_j$	$\phi_b$ (V)	$C_{jsw}$ (fF/ $\mu\text{m}$ )	$m_{jsw}$	$\phi_{bds}$ (V)
NMOS	6	0.31	2	0.5	0.9	0.28	0.44	0.9
PMOS	6	0.27	1.9	0.48	0.9	0.22	0.32	0.9


EECS141

Lecture #11

20

## Simplified Model

- Capacitance models important for analysis and intuition
  - But often need something simpler to work with
- Simple switch model:
  - Lump together as effective linear capacitance to (ac) ground
  - In most processes:  $C_G = C_D = 1.5 - 2\text{fF} \cdot W(\mu\text{m})$

 


EECS141

Lecture #11

21

## Model Calibration - Capacitance

- Can calculate  $C_g$ ,  $C_d$  based on tech. parameters
  - But these models are simplified too
- Another approach:
  - Tune (e.g., in spice) the linear capacitance until it makes the simplified circuit match the real circuit
  - Matching could be for delay, power, etc.

 


EECS141

Lecture #11


22

## Model Calibration for Delay

 

- For gate capacitance:
  - Make inverter fanout 4
  - Adjust  $C_{load}$  until Delay1 = Delay2
- For diffusion capacitance
  - Replace inverter “A” with a diffusion capacitance load


## Delay Calibration

 

- Why did we need that last inverter stage?
 
## The Miller Effect

- As  $V_{in}$  increases,  $V_{out}$  drops
  - Once get into the transition region, gain from  $V_{in}$  to  $V_{out} > 1$
- So,  $C_{gd}$  experiences voltage swing larger than  $V_{in}$ 
  - Which means you need to provide more charge
  - Makes  $C_{gd}$  look larger than it really is
- Known as the “Miller Effect” in the analog world




## CMOS Switching Delay



## MOS Transistor as a Switch


- Discharging a capacitor

 

$$i_D = i_D(v_{DS})$$

$$i_D = C \frac{dV_{DS}}{dt}$$

- We modeled this with:

 

$$t_p = \ln(2) RC$$

EECS141

Lecture #11

27

## MOS Transistor as a Switch

- Saw that real transistors aren't exactly resistors
  - Look more like current sources in saturation
- Two questions:
  - Which region of IV curve determines delay?
  - How can that match up with the RC model?



EECS141

Lecture #11

28

## Transistor Driving a Capacitor



- With a step input:

  

- Transistor is in (velocity) saturation during entire transition from  $V_{DD}$  to  $V_{DD}/2$
  
## Switching Delay


- In saturation, transistor basically acts like a current source:



$$V_{OUT} = V_{DD} - (I_{DSAT}/C)t \longrightarrow t_p = C(V_{DD}/2)/I_{DSAT}$$

## Switching Delay (with Output Conductance)

- Including output conductance:

 


$$V_{OUT} = (V_{DD} + \lambda^{-1}) e^{-t/(C/\lambda I_{DSAT})} - \lambda^{-1}$$

- For “small”  $\lambda$ :

$$t_p \approx \frac{C(V_{DD}/2)}{(1 + \lambda V_{DD}) I_{DSAT}}$$
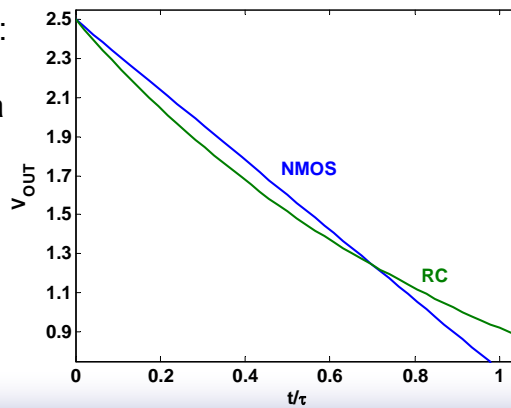
## RC Model

- Transistor current not linear on  $V_{OUT}$  – how is the RC model going to work?
- Look at waveforms:
- Voltage looks like a ramp for RC too





## Finding Req

- Match the delay of the RC model with the actual delay:

$$t_p = t_{p,RC}$$

$$\frac{C(V_{DD}/2)}{(1 + \lambda V_{DD}) I_{DSAT}} = \ln(2) R_{eq} C \quad \longrightarrow \quad R_{eq} = \frac{(V_{DD}/2)}{\ln(2)(1 + \lambda V_{DD}) I_{DSAT}}$$


- Often just:

$$R_{eq} \approx \frac{1}{2 \cdot \ln(2)} \frac{V_{DD}}{I_{DSAT}}$$

- Note that the book uses a different method and gets  $0.75 \cdot V_{DD}/I_{DSAT}$  instead of  $\sim 0.72 \cdot V_{DD}/I_{DSAT}$ 
  - Why did we do it this way vs. the book's method?

## The Book's Method

## The Transistor as a Switch

 

EECS141

Lecture #11

35

## The Transistor as a Switch

**Table 3.3** Equivalent resistance  $R_{eq}$  ( $W/L = 1$ ) of NMOS and PMOS transistors in 0.25  $\mu\text{m}$  CMOS process (with  $L = L_{min}$ ). For larger devices, divide  $R_{eq}$  by  $W/L$ .

$V_{DD}$ (V)	1	1.5	2	2.5
NMOS (k $\Omega$ )	35	19	15	13
PMOS (k $\Omega$ )	115	55	38	31

EECS141

Lecture #11

36