


*EE141-Fall 2012
Digital Integrated
Circuits*

Lecture 11
MOS Capacitance
and Delay

EECS141 Lecture #11 1

MOS Capacitance




EECS141 Lecture #11 4

Announcements

- No labs this week
 - Labs restart next week
- Midterm #1 Thurs. Oct. 4th, 6:30-8:00pm
 - Exam is open notes, book, calculators, etc.
 - Covers up to lecture 10

EECS141 Lecture #11 2

MOS Capacitances

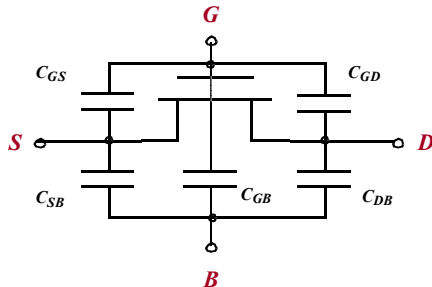

EECS141 Lecture #11 5

Class Material

- Last lecture
 - Using the MOS model: Inverter VTC
- Today's lecture
 - MOS Capacitance
 - Using the MOS Model: Delay
- Reading (3.3.2, 5.4.2)

EECS141 Lecture #11 3

Gate Capacitance


- Capacitance (per area) from gate across the oxide is $W \cdot L \cdot C_{ox}$, where $C_{ox} = \epsilon_{ox} / t_{ox}$
 - But channel isn't really a terminal in my MOS transistor model...

EECS141 Lecture #11 6

Gate Capacitance


- Distribution between terminals is complex
 - Capacitance is really distributed
 - Useful models lump it to the terminals
 - Several operating regions:
 - Way off, off, transistor linear, transistor saturated

Transistor in Linear Region

 


- Channel is formed and acts as the other terminal
 - C_{GCB} drops to zero (shielded by channel)
- Model by splitting oxide cap equally between source and drain
 - Changing either voltage changes the channel charge

Transistor In Cutoff

 


- When the transistor is off, no carriers in channel to form the other side of the capacitor.
 - Substrate acts as the other capacitor terminal
 - Capacitance becomes series combination of gate oxide and depletion capacitance

Transistor in Saturation Region

 


- Changing source voltage doesn't change V_{GC} uniformly
 - E.g. V_{GC} at pinch off point still V_{TH}
- Bottom line: $C_{GCS} \approx 2/3 \cdot W \cdot L \cdot C_{ox}$

Transistor In Cutoff (cont'd)

 

- When $|V_{GS}| < |V_{TH}|$, total C_{GCB} much smaller than $W \cdot L \cdot C_{ox}$
 - Usually just approximate with $C_{GCB} = 0$ in this region.
- (If V_{GS} is "very" negative (for NMOS), depletion region shrinks and C_{GCB} goes back to $\sim W \cdot L \cdot C_{ox}$)

Transistor in Saturation Region (cont'd)

 

- Drain voltage no longer affects channel charge
 - Set by source and V_{DS_sat}
- If change in charge is 0, $C_{GCD} = 0$

Gate Capacitance

$C_{\text{gate vs. } V_{GS}}$ (with $V_{DS} = 0$)

$C_{\text{gate vs. operating region}}$

EECS141 Lecture #11 13

Diffusion Capacitance

- Bottom
 - Area cap
 - $C_{\text{bottom}} = C_j \cdot L_S \cdot W$
- Sidewalls
 - Perimeter cap
 - $C_{\text{sw}} = C_{j\text{sw}} \cdot (2L_S + W)$
- GateEdge
 - $C_{\text{ge}} = C_{j\text{gate}} \cdot W$
 - Usually automatically included in the SPICE model

EECS141 Lecture #11 16

Gate Overlap Capacitance

$C_O = C_{ox} \cdot x_d$

Off/Lin/Sat $\rightarrow C_{GSO} = C_{GDO} = C_O \cdot W$

EECS141 Lecture #11 14

Junction Capacitance (2)

- Junction caps are nonlinear
 - C_j is a function of junction bias
- SPICE model equations:
 - Area $C_j = \text{area} \times C_{j0} / (1 + |V_{DB}|/\phi_b)^m$
 - Perimeter $C_j = \text{perim} \times C_{j\text{sw}} / (1 + |V_{DB}|/\phi_b)^m$
 - Gate edge $C_j = W \times C_{j\text{gate}} / (1 + |V_{DB}|/\phi_b)^m$
- How do we deal with nonlinear capacitance?

EECS141 Lecture #11 17

Gate Fringe Capacitance

- C_{OV} not just from metallurgic overlap – get fringing fields too
- Typical value: $\sim 0.2\text{fF} \cdot W(\text{in } \mu\text{m})/\text{edge}$

EECS141 Lecture #11 15

Linearizing the Junction Capacitance

Replace non-linear capacitance by large-signal equivalent linear capacitance which displaces equal charge over voltage swing of interest

$$C_{eq} = \frac{\Delta Q_j}{\Delta V_D} = \frac{Q_j(V_{high}) - Q_j(V_{low})}{V_{high} - V_{low}} = K_{eq} C_{j0}$$

$$K_{eq} = \frac{-\phi_b^m}{(V_{high} - V_{low})(1 - m)} [(\phi_b - V_{high})^{1-m} - (\phi_b - V_{low})^{1-m}]$$

EECS141 Lecture #11 18

Capacitance Model Summary

Gate-Channel Capacitance

- $C_{GC} \approx 0$ ($|V_{GS}| < |V_{T1}|$) (Linear)
- $C_{GC} = C_{ox} \cdot W \cdot L_{eff}$ (Linear)
– 50% G to S, 50% G to D
- $C_{GC} = (2/3) \cdot C_{ox} \cdot W \cdot L_{eff}$ (Saturation)
– 100% G to S

Gate Overlap Capacitance

- $C_{GSO} = C_{GDO} = C_O \cdot W$ (Always)

Junction/Diffusion Capacitance

- $C_{diff} = C_j \cdot L_S \cdot W + C_{jsw} \cdot (2L_S + W) + C_{jg} W$ (Always)


EECS141

Lecture #11

19

Model Calibration - Capacitance

- Can calculate C_g, C_d based on tech. parameters
– But these models are simplified too
- Another approach:
– Tune (e.g., in spice) the linear capacitance until it makes the simplified circuit match the real circuit
– Matching could be for delay, power, etc.

 

EECS141

Lecture #11

22

Capacitances in 0.25 μm CMOS Process


	C_{ox} (fF/ μm^2)	C_O (fF/ μm)	C_j (fF/ μm^2)	m_j	ϕ_b (V)	C_{jsw} (fF/ μm)	m_{jsw}	ϕ_{jsw} (V)
NMOS	6	0.31	2	0.5	0.9	0.28	0.44	0.9
PMOS	6	0.27	1.9	0.48	0.9	0.22	0.32	0.9

EECS141

Lecture #11

20

Model Calibration for Delay

 

- For gate capacitance:
– Make inverter fanout 4
– Adjust C_{load} until Delay1 = Delay2
- For diffusion capacitance
– Replace inverter "A" with a diffusion capacitance load


EECS141

Lecture #11

23

Simplified Model

- Capacitance models important for analysis and intuition
– But often need something simpler to work with
- Simple switch model:
– Lump together as effective linear capacitance to (ac) ground
– In most processes: $C_G = C_D = 1.5 - 2\text{fF} \cdot W(\mu\text{m})$

 


EECS141

Lecture #11

21

Delay Calibration

 

- Why did we need that last inverter stage?


EECS141

Lecture #11

24

The Miller Effect

 - As V_{in} increases, V_{out} drops
 - Once get into the transition region, gain from V_{in} to $V_{out} > 1$
- So, C_{gd} experiences voltage swing larger than V_{in}
 - Which means you need to provide more charge
 - Makes C_{gd} look larger than it really is
- Known as the "Miller Effect" in the analog world



MOS Transistor as a Switch


- Saw that real transistors aren't exactly resistors
 - Look more like current sources in saturation
- Two questions:
 - Which region of IV curve determines delay?
 - How can that match up with the RC model?

CMOS Switching Delay



Transistor Driving a Capacitor


- With a step input:

 

- Transistor is in (velocity) saturation during entire transition from V_{DD} to $V_{DD}/2$

MOS Transistor as a Switch


- Discharging a capacitor

 

$$i_D = i_D(V_{DS})$$

$$i_D = C \frac{dV_{DS}}{dt}$$


- We modeled this with:

 

$$t_p = \ln(2) RC$$

Switching Delay

 
- In saturation, transistor basically acts like a current source:



$$V_{OUT} = V_{DD} - (I_{DSAT}/C)t \longrightarrow t_p = C(V_{DD}/2)/I_{DSAT}$$

Switching Delay (with Output Conductance)

- Including output conductance:

 


$$V_{OUT} = (V_{DD} + \lambda^{-1}) e^{-t/(C/\lambda I_{DSAT})} - \lambda^{-1}$$

- For "small" λ :
$$t_p \approx \frac{C(V_{DD}/2)}{(1 + \lambda V_{DD}) I_{DSAT}}$$


The Book's Method

RC Model

 - Transistor current not linear on V_{OUT} – how is the RC model going to work?
- Look at waveforms:
- Voltage looks like a ramp for RC too



The Transistor as a Switch

 

Finding Req

- Match the delay of the RC model with the actual delay:

$$\frac{C(V_{DD}/2)}{(1 + \lambda V_{DD}) I_{DSAT}} = \ln(2) R_{eq} C \rightarrow R_{eq} = \frac{(V_{DD}/2)}{\ln(2)(1 + \lambda V_{DD}) I_{DSAT}}$$

- Often just:
$$R_{eq} \approx \frac{1}{2 \cdot \ln(2)} \frac{V_{DD}}{I_{DSAT}}$$

- Note that the book uses a different method and gets $0.75 \cdot V_{DD} / I_{DSAT}$ instead of $\sim 0.72 \cdot V_{DD} / I_{DSAT}$
- Why did we do it this way vs. the book's method?

The Transistor as a Switch

Table 3.3 Equivalent resistance R_{eq} ($W/L = 1$) of NMOS and PMOS transistors in 0.25 μm CMOS process (with $L = L_{min}$). For larger devices, divide R_{eq} by W/L .

V_{DD} (V)	1	1.5	2	2.5
NMOS (k Ω)	35	19	15	13
PMOS (k Ω)	115	55	38	31