

EE141-Fall 2012 Digital Integrated Circuits

Lecture 12 CMOS Delay and Power Models

Announcements


- Midterm #1 Thurs., 6:30-8:00pm, 141 McCone
 - Be sure to arrive on time
- Midterm review session today, 6pm, 550 Cory
- Lecture will be “taped-ahead” for this Thurs..
- Homework #6 out this Thurs., due next Thurs.

Class Material

- Last lecture
 - MOS Capacitance, delay
- Today's lecture
 - Improved CMOS Delay and Power Models
- Reading (5.1-5.3, 5.4.2)

Propagation Delay



 


Step Inputs?

- Derived RC model assuming input was a step
 - But input is not a step
 - Transistor turns on gradually

- Let's look at gate switching more carefully
 - Use our models to understand the effect of input slope

EECS141 Lecture #12 6

Input Slope Dependence

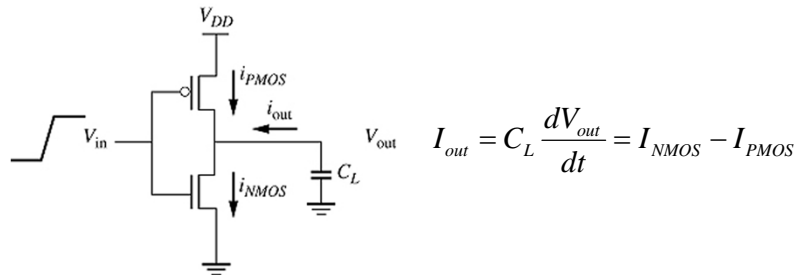

- One way to analyze slope effect
 - Plug non-linear IV into diff. equation and solve...
- Simpler, approximate solution:
 - Use V_T^* model

Slope Analysis

- For falling edge at output:
 - For reasonable inputs, can ignore I_{PMOS}
 - Either V_{ds} is very small, or V_{gs} is very small
- So, output current ramp starts when $V_{in} = V_T^*$
 - Could evaluate the integral implied by slide 7
 - Learn more by using an intuitive, graphical approach

Slope Effect

EECS141

Lecture #12

9

Slope Effect

EECS141

Lecture #12

10

Result Summary


- For reasonable input slopes:

$$t_{p,ramp} = t_{p,step} + \frac{V_T^*}{V_{DD}} \cdot t_{p,in}$$

- For $t_{p,avg}$, V_T^* is $(V_{TN}^* + V_{TP}^*)/2$
 - V_T^*/V_{DD} typically $\sim 1/3$ at nominal supply

Model vs. Spice Data

 - For reasonable input slope
 - Model matches Spice very well
- Model breaks with very large t_r
 - Input looks “DC” – traces out VTC
 - Have other problems here anyways
 - Short-circuit current



Implications

- Delay of an inverter after a long chain:

Implications

CMOS Power Dissipation



EECS141

Lecture #12

15

Where Does Power Go in CMOS?


- ❑ Switching power
 - Charging/discharging capacitors
- ❑ Leakage power
 - Transistors are imperfect switches
- ❑ Short-circuit power
 - Both pull-up and pull-down on during transition
- ❑ Static currents
 - Biasing currents, in e.g. analog, memory

EECS141

Lecture #12


16

Dynamic Power Consumption

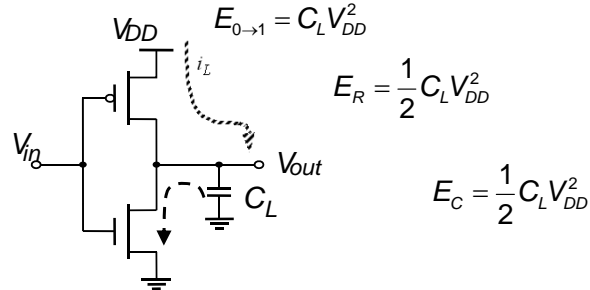

- One half of the energy from the supply is consumed in the pull-up network, one half is stored on C_L
- Energy from C_L is dumped during the $1 \rightarrow 0$ transition

Circuits with Reduced Swing

 

$$E_{0 \rightarrow 1} =$$

Dynamic Power Consumption

Power = Energy/transition • (Transition rate/2)
 = Energy/transition • (Rising transition rate)

$$= C_L V_{DD}^2 \cdot f_{0 \rightarrow 1}$$

$$= C_L V_{DD}^2 \cdot f \cdot P_{0 \rightarrow 1}$$

$$= C_{switched} V_{DD}^2 \cdot f$$

- Power dissipation is data dependent – depends on the switching probability
- Switched capacitance $C_{switched} = C_L \cdot P_{0 \rightarrow 1}$

Transition Activity and Power

- Energy consumed in N cycles, E_N :

$$E_N = C_L \cdot V_{DD}^2 \cdot n_{0 \rightarrow 1}$$

$n_{0 \rightarrow 1}$ – number of 0→1 transitions in N cycles

$$P_{avg} = \lim_{N \rightarrow \infty} \frac{E_N}{N} \cdot f = \left(\lim_{N \rightarrow \infty} \frac{n_{0 \rightarrow 1}}{N} \right) \cdot C_L \cdot V_{DD}^2 \cdot f$$

$$\alpha_{0 \rightarrow 1} = \lim_{N \rightarrow \infty} \frac{n_{0 \rightarrow 1}}{N}$$

$$P_{avg} = \alpha_{0 \rightarrow 1} \cdot C_L \cdot V_{DD}^2 \cdot f$$

Short Circuit Current

Large load

Small load

□ Short circuit current usually well controlled

EECS141
Lecture #12
21

Transistor Leakage


□ Transistors that are supposed to be off actually leak

Input at V_{DD}

Input at 0

EECS141
Lecture #12
22


Diode Leakage

 

$$I_{DL} = J_S \times A$$


$J_S = 10\text{-}100 \text{ pA}/\mu\text{m}^2$ at 25 deg C for $0.25\mu\text{m}$ CMOS
 J_S doubles for every 9 deg C!
 Much smaller than transistor leakage in deep submicron

Transistor Leakage

 

Drain leakage current is exponential with $V_{GS} - V_T$

Sub-Threshold Conduction

 

Inverse Subthreshold Slope:


$$I_D \sim I_0 e^{\frac{q(V_{GS}-V_T)}{nkT}}, \quad n = 1 + \frac{C_D}{C_{ox}}$$

S^{-1} is ΔV_{GS} for $I_{D2}/I_{D1} = 10$

$$S^{-1} = n \left(\frac{kT}{q} \right) \ln(10)$$

Typical values for S^{-1} :
60 .. 100 mV/decade

Transistor Leakage vs. V_{DS}

 


$$I_D = \frac{W}{L} I_0 e^{\frac{q(V_{GS} - (V_T - \eta V_{DS}))}{nkT}} \left(1 - e^{-\frac{qV_{DS}}{kT}} \right)$$


Two effects:

- diffusion current (like a bipolar transistor)
- exponential increase with V_{DS} (η : DIBL)

Threshold Variations

 

 Threshold as a function of length (for low V_{DS})



Drain-induced barrier lowering (DIBL) (for short L)

Power Summary

Next Lecture

- CMOS Logic Review