




*EE141-Fall 2012  
Digital Integrated  
Circuits*

Lecture 13  
CMOS Logic Review

EECS141 Lecture #13 1



*CMOS Logic  
Review*

EECS141 Lecture #13 4

*Announcements*

- Midterm tonight 6:30pm sharp
- Homework #6 out tonight, due next Thurs.
- Reminder:
  - Project coming up in 2 weeks – find a partner

EECS141 Lecture #13 2

*Cell Design*

- Standard Cells
  - General purpose logic
  - Used to synthesize RTL/HDL
  - Same height, varying width
- Datapath Cells
  - For regular, structured designs (arithmetic)
  - Includes some wiring in the cell


EECS141 Lecture #13 5

*Class Material*

- Last lecture
  - CMOS Delay and Power Models
- Today's lecture
  - CMOS Logic Review
- Reading (6)

EECS141 Lecture #13 3

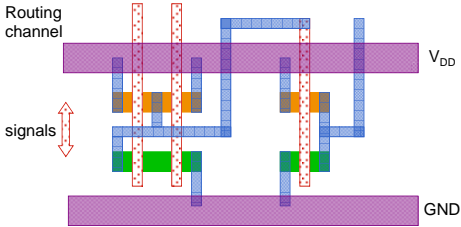*Standard Cell Layout Methodology –  
1980s*



EECS141 Lecture #13 6

### Standard Cell Layout Methodology - 1990s - Today

Mirrored Cell

No routing channels

$V_{DD}$

$V_{DD}$

M2

M3

GND

GND

Mirrored Cell

EECS141 Lecture #13 7

### Stick Diagrams

Contains no dimensions  
Represents relative positions of transistors

Inverter

$V_{DD}$

GND

In

Out

NAND2

$V_{DD}$

GND

A

B

Out

EECS141 Lecture #13 10

### Standard Cells

N Well

$V_{DD}$

Cell height 12 metal tracks  
Metal track is approx.  $3\lambda + 3\lambda$   
Pitch = repetitive distance between objects  
Cell height is "12 Mn pitch"

$2\lambda$

In

Out

GND

Cell boundary

Rails  $\sim 10\lambda$

EECS141 Lecture #13 8

### Stick Diagrams

How to lay this gate out to minimize area?

A

B

C

F

C

$X = C \cdot (A + B)$

A

B

C

EECS141 Lecture #13 11

### Standard Cells

With minimal diffusion routing

$V_{DD}$

$V_{DD}$

In

Out

GND

GND

With silicided diffusion

$V_{DD}$

$V_{DD}$

In

Out

GND

GND

$V_{DD}$

In

Out

GND

GND

EECS141 Lecture #13 9

### Two Versions of $C \cdot (A + B)$

A

C

B

$V_{DD}$

GND

X

A

B

C

$V_{DD}$

GND


X

EECS141 Lecture #13 12

### Consistent Euler Path

A B C  
Has PDN and PUP

B C A  
Has PUP, but no PDN

 


### Multi-Fingered Transistors

How can you fit wide transistors into a fixed height?



One finger

Two fingers (folded)

 


Less diffusion capacitance

### OAI22 Logic Graph

 
 


### Fan-In Considerations


RC model:

 

### Example: $x = ab+cd$

  


### Fan-In Considerations

 

Distributed RC model (Elmore delay)

$$t_{pHL} = 0.69 R_{eqn}(C_1+2C_2+3C_3+4C_L)$$

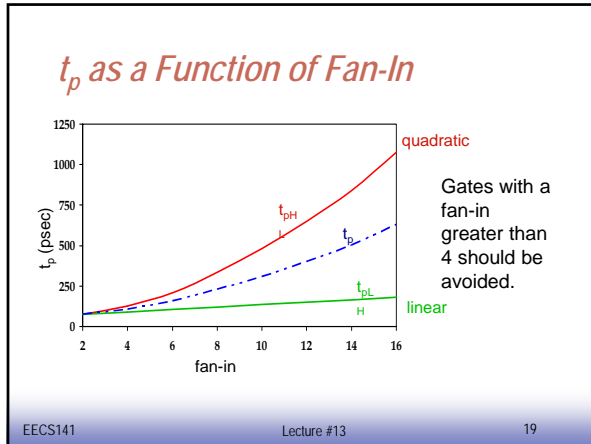Propagation delay deteriorates rapidly as a function of fan-in – quadratically in the worst case.




### Reducing Delay (3)

- Reducing the voltage swing
 
$$t_{pHL} = 0.5 (C_L V_{DD}) / I_{DSATn}$$


$$= 0.5 (C_L V_{swing}) / I_{DSATn}$$
  - linear reduction in delay
  - also reduces power consumption
- But the following gate is slower!
- Or requires use of “sense amplifiers” on the receiving end to restore the signal level (memory design)

EECS141 Lecture #13 22

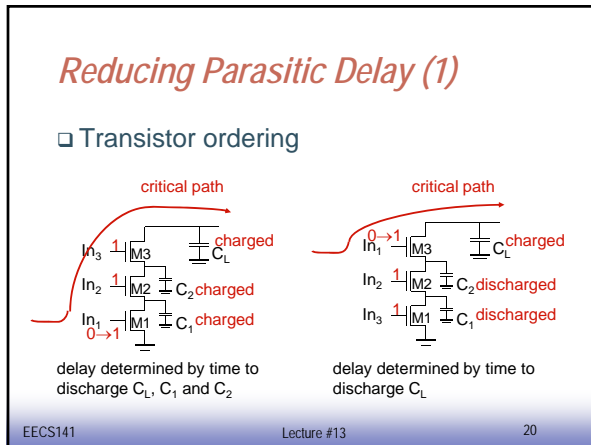

### LE in Modern Processes

EECS141 Lecture #13 23

 

### LE in Modern Processes

EECS141 Lecture #13 24

*Next Lecture*

- Wires