

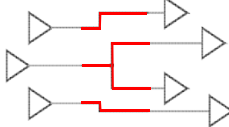



*EE141-Fall 2012  
Digital Integrated  
Circuits*

Lecture 14  
Wires

EECS141      Lecture #14      1

*The Wire*

Schematic      Physical


EECS141      Lecture #14      4

*Announcements*

- Homework #6 due this Thurs.
  - Homework #7 out this Thurs.
- Project #1 out Oct. 18<sup>th</sup>
  - Find a partner


EECS141      Lecture #14      2

*Wire Models*

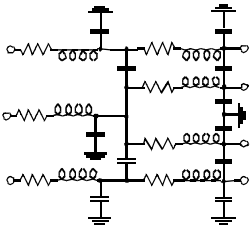

EECS141      Lecture #14      5

*Wires*



EECS141      Lecture #14      3

*Impact of Interconnect Parasitics*

- Interconnect and its parasitics can affect all of the metrics we care about
  - Cost, reliability, performance, power consumption
- Parasitics associated with interconnect:
  - Capacitance
  - Resistance
  - Inductance

EECS141      Lecture #14      6


# INTERCONNECT

# Capacitance




EECS141      Lecture #14      7

## Fringing Capacitance
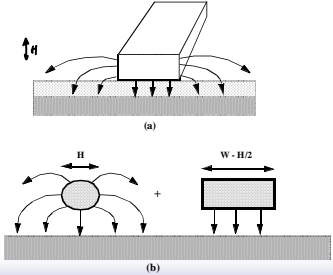
$$c_{wire} = c_{pp} + c_{fringe} = \frac{w\epsilon_{di}}{t_{di}} + \frac{2\pi\epsilon_{di}}{\log(t_{di}/H)}$$


EECS141      Lecture #14      10


## Capacitance: The Parallel Plate Model

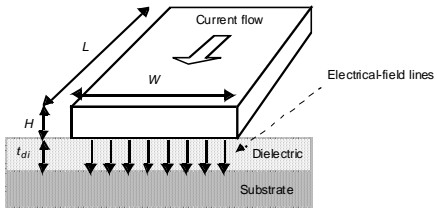

$$c_{int} = \frac{\epsilon_{di}}{t_{di}} WL$$

EECS141      Lecture #14      8

## Fringing versus Parallel Plate

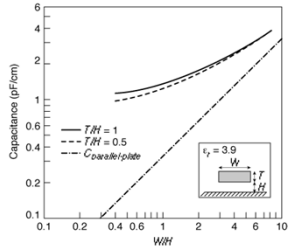

(from [Bakoglu89])


EECS141      Lecture #14      11

## Permittivity

Material	$\epsilon_r$
Free space	1
Aerogels	~1.5
Polyimides (organic)	3-4
Silicon dioxide	3.9
Glass-epoxy (PC board)	5
Silicon Nitride ( $Si_3N_4$ )	7.5
Alumina (package)	9.5
Silicon	11.7


EECS141      Lecture #14      9

## Interwire Capacitance

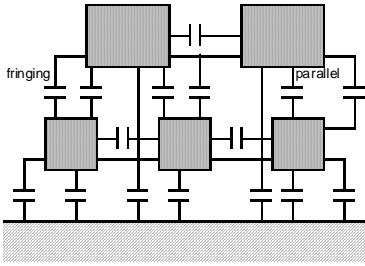

EECS141      Lecture #14      12

### Coupling Capacitance and Delay

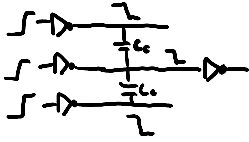


$$C_{c,eff} =$$

EECS141

Lecture #14

13

### Impact of Interwire Capacitance

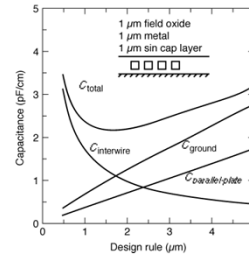


(from [Bakoglu89])

EECS141

Lecture #14

16

### Coupling Capacitance and Delay

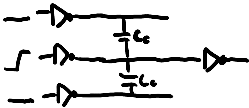

$$C_{c,eff} =$$

EECS141

Lecture #14

14

### Wiring Capacitances (0.25 μm CMOS)

Bottom plate

	Field	Active	Poly	Al1	Al2	Al3	Al4
Poly	88	9F/μm <sup>2</sup>					
	54	9F/μm <sup>2</sup>					
Al1	30	41	57				
	40	47	54				
Al2	13	15	17	36			
	25	27	29	45			
Al3	8.9	9.4	10	15	41		
	18	19	20	27	49		
Al4	6.5	6.8	7	8.9	15	35	
	14	15	15	18	27	45	
Al5	5.2	5.4	5.4	6.6	9.1	14	38
	12	12	12	14	19	27	52


Top plate

EECS141

Lecture #14

17

### Coupling Capacitance and Delay

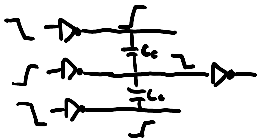


$$C_{c,eff} =$$

EECS141

Lecture #14

15

### Wiring Capacitances

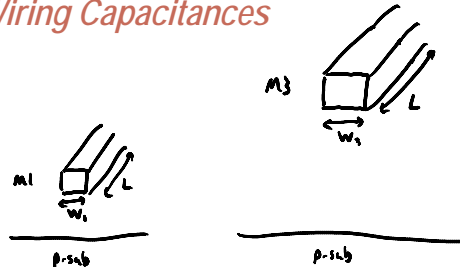

$$C = C_{pp} \cdot W \cdot L + 2C_{fringe} L$$

EECS141

Lecture #14

18

## INTERCONNECT




EECS141      Lecture #14      19

## Example Numbers

Material	Sheet Resistance ( $\Omega/\square$ )
n- or p-well diffusion	1000 – 1500
$n^+, p^+$ diffusion	50 – 150
$n^+, p^+$ diffusion with silicide	3 – 5
$n^+, p^+$ polysilicon	150 – 200
$n^+, p^+$ polysilicon with silicide	4 – 5
Aluminum	0.05 – 0.1


EECS141      Lecture #14      22

## Wire Resistance

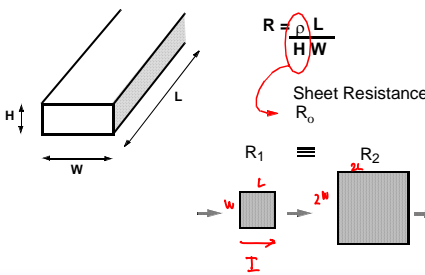

$R = \frac{\rho L}{HW}$   
 Sheet Resistance  $R_0$   
 $R_1$      $R_2$

EECS141      Lecture #14      20



## Interconnect Modeling

EECS141      Lecture #14      23


## Dealing with Resistance

Better materials:       More layers:

Material	$\rho$ ( $\Omega\text{-m}$ )
Silver (Ag)	$1.6 \times 10^{-8}$
Copper (Cu)	$1.7 \times 10^{-8}$
Gold (Au)	$2.2 \times 10^{-8}$
Aluminum (Al)	$2.7 \times 10^{-8}$
Tungsten (W)	$5.5 \times 10^{-8}$

EECS141      Lecture #14      21


## The Distributed RC-line

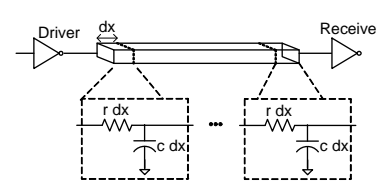

- Analysis method:
  - Break the wire up into segments of length  $dx$
  - Each segment has resistance ( $r dx$ ) and capacitance ( $c dx$ )

EECS141      Lecture #14      24

### The Distributed RC-line

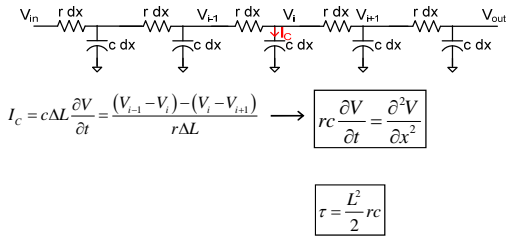

### Wire Delay Example

### Wire Model

Model the wire with N equal-length segments:

$$\tau_{DN} = \left(\frac{L}{N}\right)^2 (rc + 2rc + \dots + Nrc) = (rcL^2) \frac{N(N+1)}{2N^2} = RC \frac{N+1}{2N}$$

For large values of N:

$$\tau_{DN} = \frac{RC}{2} = \frac{rcL^2}{2}$$

### Next Lecture

□ SRAM Circuit Design

### RC-Models

Voltage Range	Lumped RC-network	Distributed RC-network
0-50% ( $t_p$ )	0.69 RC	0.38 RC
0-63% ( $\tau$ )	RC	0.5 RC
10%-90% ( $t_r$ )	2.2 RC	0.9 RC

Step Response of Lumped and Distributed RC Networks:  
Points of Interest.

