


*EE141-Fall 2010
Digital Integrated
Circuits*

Lecture 15
SRAM Circuit Design

Announcements


- Homework #6 due today
 - Homework #7 due next Thurs.
 - Project #1 out next Thurs.



SRAM Circuit Design


EECS141
Lecture #15
3

6-transistor CMOS SRAM Cell

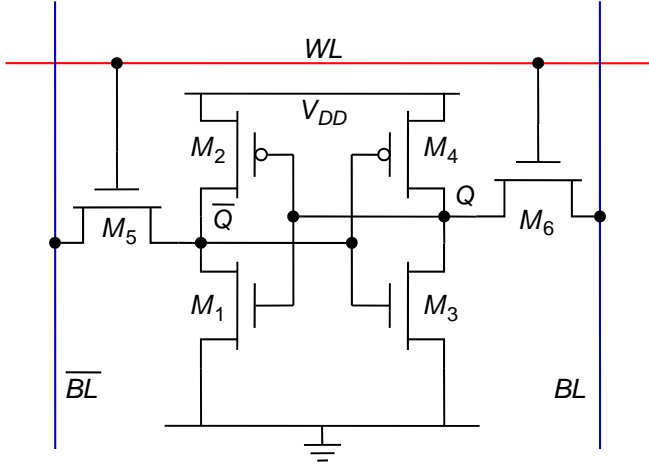


EECS141
Lecture #15
4

SRAM Column

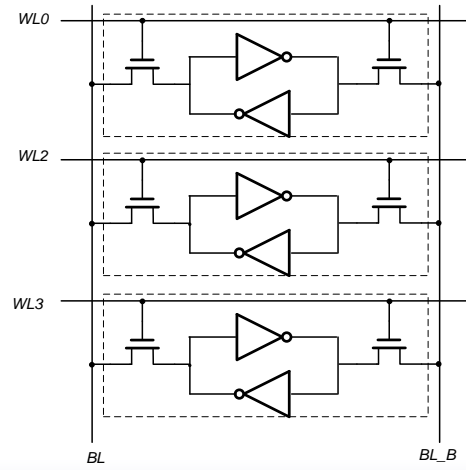


SRAM Operation

Write

 


Hold

 


SRAM Operation

Read

 

- Q_b will get pulled up when WL first goes high
- Reading the cell should not destroy the stored value


CMOS SRAM Analysis (Read)

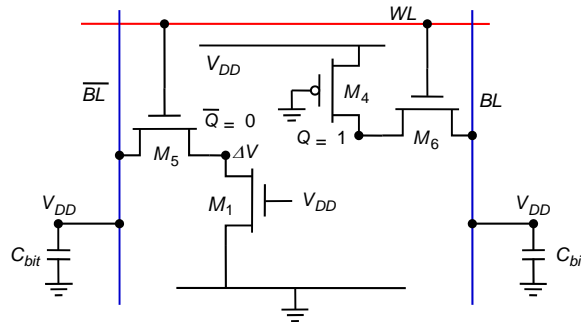

$$I_{D5} = I_{D1}$$


$$W_5 V_{sat} C_{ox} \frac{(V_{DD} - V_{Tn} - \Delta V)^2}{V_{DD} - V_{Tn} - \Delta V + \xi_{crit,n} L_5} = \mu_n C_{ox} \frac{W_1}{L_1} \left(V_{DD} - V_{Tn} - \frac{\Delta V}{2} \right) \Delta V$$

CMOS SRAM Analysis (Read)

 


$$CR = \frac{W_1/L_1}{W_5/L_5}$$

CMOS SRAM Analysis (Write)

 


$$W_4 v_{sat} C_{ox} \frac{(V_{DD} - V_{Tp})^2}{V_{DD} - V_{Tp} + \xi_{crit,p} L_4} = \mu_n C_{ox} \frac{W_6}{L_6} \left(V_{DD} - V_{Tn} - \frac{V_Q}{2} \right) V_Q$$



CMOS SRAM Analysis (Write)

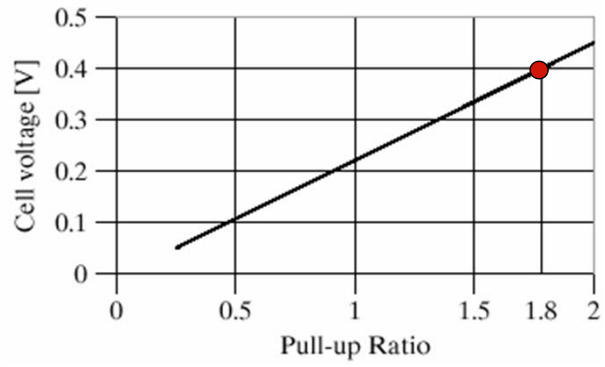

$$PR = \frac{(W/L)_4}{(W/L)_6}$$

Read Static Noise Margin

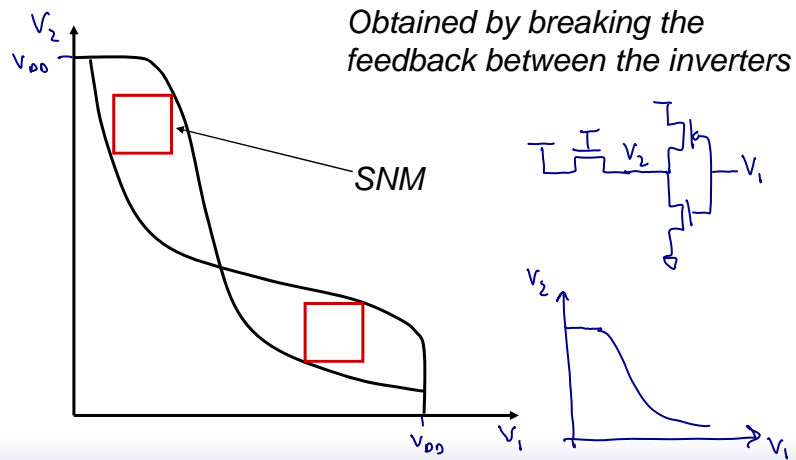

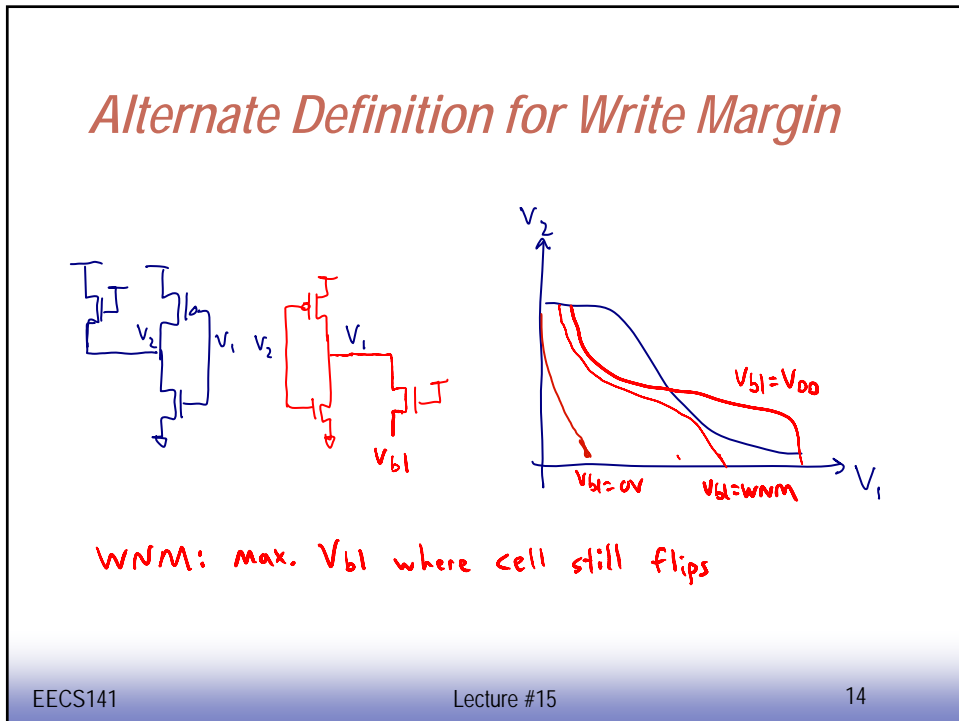 

Next Lecture

- Power Revisited