



## *EE141-Fall 2012 Digital Integrated Circuits*

Lecture 16  
Power Revisited

## *Announcements*

- Homework #7 due Thursday
  - Project #1 due next Thurs.
  
- Midterm 2: Thurs. Nov. 1<sup>st</sup>, 6:30-8:00pm, room TBA
  
- Find a project partner



## *Power Revisited*

EECS141

Lecture #16

3

## *Transition Activity and Power*

- Energy consumed in  $N$  cycles,  $E_N$ :

$$E_N = C_L \cdot V_{DD}^2 \cdot n_{0 \rightarrow 1}$$

$n_{0 \rightarrow 1}$  – number of 0→1 transitions in  $N$  cycles

$$P_{avg} = \lim_{N \rightarrow \infty} \frac{E_N}{N} \cdot f = \left( \lim_{N \rightarrow \infty} \frac{n_{0 \rightarrow 1}}{N} \right) \cdot C_L \cdot V_{DD}^2 \cdot f$$

$$\alpha_{0 \rightarrow 1} = \lim_{N \rightarrow \infty} \frac{n_{0 \rightarrow 1}}{N} \cdot f$$

$$P_{avg} = \alpha_{0 \rightarrow 1} \cdot C_L \cdot V_{DD}^2 \cdot f$$

EECS141

Lecture #16

4

## Factors Affecting Transition Activity

- “Static” component (does not account for timing)
  - ← Type of Logic Function (NOR vs. XOR)
  - ← Type of Logic Style (Static vs. Dynamic)
  - ← Signal Statistics
  - ← Inter-signal Correlations
- “Dynamic” or timing dependent component
  - ← Circuit Topology
  - ← Signal Statistics and Correlations

## Type of Logic Function: NOR

Example: Static 2-input NOR Gate

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Assume signal probabilities

$$p_{A=1} = 1/2$$

$$p_{B=1} = 1/2$$

Then transition probability

$$p_{0 \rightarrow 1} = p_{Out=0} \times p_{Out=1}$$

$$= 3/4 \times 1/4 = 3/16$$

If inputs switch every cycle

$$\alpha_{0 \rightarrow 1} = 3/16$$

## Type of Logic Function: NAND

Example: Static 2-input NAND Gate

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Assume **signal probabilities**

$$p_{A=1} = 1/2$$

$$p_{B=1} = 1/2$$

Then **transition probability**

$$p_{0 \rightarrow 1} = p_{Out=0} \times p_{Out=1}$$

$$= 3/4 \times 1/4 = 3/16$$

If inputs switch every cycle

$$\alpha_{0 \rightarrow 1} = 3/16$$

## Type of Logic Function: XOR

Example: Static 2-input XOR Gate

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

Assume **signal probabilities**

$$p_{A=1} = 1/2$$

$$p_{B=1} = 1/2$$

Then **transition probability**

$$p_{0 \rightarrow 1} = p_{Out=0} \times p_{Out=1}$$

=


If inputs switch in every cycle

$$\alpha_{0 \rightarrow 1} =$$

## *Clock*

- Always switches
- Often consumes 25-50% of total power
- Clock gating commonly employed


## *Problem: Reconvergent Fanout*

 

$$P(Z = 1) = P(B = 1) \cdot P(X = 1 \mid B=1)$$


**Becomes complex and intractable fast**

## Inter-Signal Correlations

 

Logic without reconvergent fanout
 
$$p_{0 \rightarrow 1} = (1 - p_{\bar{A}} p_B) p_{\bar{A}} p_B$$





Logic with reconvergent fanout

$$P(Z = 1) = p(C=1 | B=1) p(B=1)$$

$$p_{0 \rightarrow 1} = 0$$

- Need to use conditional probabilities to model inter-signal correlations
- CAD tools best for performing such analysis

## Glitching in Static CMOS

  

Also known as dynamic hazards

The result is correct,  
but there is extra power dissipated

## *Principles for Power Reduction*


- Most important idea: reduce waste
- Examples:
  - Don't switch capacitors you don't need to
    - Clock gating, glitch elimination, logic re-structuring
  - Don't run circuits faster than needed
    - Power  $\propto V_{DD}^2$  – can save a lot by reducing supply for circuits that don't need to be as fast
- Let's say we do a good job of that – then what?

EECS141

Lecture #16

13

## *Energy – Performance Space*

 


- Plot all possible designs on a 2-D plane
  - No matter what you do, can never get below/to the right of the solid line
- This line is called “Pareto Optimal Curve”
  - Usually (always) follows law of diminishing returns

EECS141

Lecture #16

14

## Optimization Perspective

 

- Instead of metrics like EDP, this curve often provides information more directly
  - Ex1: What is minimum energy for XX performance?
  - Ex2: Over what range of performance is a new technique (dotted line) actually beneficial?

EECS141

Lecture #16

15

## Key Observation

- Define the Energy/Performance sensitivity of a parameter, for example:

$$S_{V_{DD}} = \frac{\partial \text{Energy} / \partial V_{DD}}{\partial \text{Perf} / \partial V_{DD}} \quad S_{V_T} = \frac{\partial \text{Energy} / \partial V_T}{\partial \text{Perf} / \partial V_T}$$

- At optimal point, sensitivities to all parameters should be the same (ignoring constraints)
  - Must equal slope of the Pareto optimal curve
  - Otherwise, could trade one parameter for another and end up with lower energy at same performance

EECS141

Lecture #16

16



## *Sensitivity Example*

EECS141

Lecture #16

17

## *Sensitivity Example*

EECS141

Lecture #16

18

## *Sensitivity Example*

## *Next Lecture*

- CMOS Scaling