



*EE141-Fall 2012
Digital Integrated
Circuits*

Lecture 16
Power Revisited

EECS141 Lecture #16 1

Transition Activity and Power

□ Energy consumed in N cycles, E_N :

$$E_N = C_L \cdot V_{DD}^2 \cdot n_{0 \rightarrow 1}$$

$n_{0 \rightarrow 1}$ – number of 0→1 transitions in N cycles

$$P_{avg} = \lim_{N \rightarrow \infty} \frac{E_N}{N} \cdot f = \left(\lim_{N \rightarrow \infty} \frac{n_{0 \rightarrow 1}}{N} \right) \cdot C_L \cdot V_{DD}^2 \cdot f$$

$$\alpha_{0 \rightarrow 1} = \lim_{N \rightarrow \infty} \frac{n_{0 \rightarrow 1}}{N} \cdot f$$

$$P_{avg} = \alpha_{0 \rightarrow 1} \cdot C_L \cdot V_{DD}^2 \cdot f$$

EECS141 Lecture #16 4

Announcements


- Homework #7 due Thursday
 - Project #1 due next Thurs.
- Midterm 2: Thurs. Nov. 1st, 6:30-8:00pm, room TBA
- Find a project partner

EECS141 Lecture #16 2

Factors Affecting Transition Activity

- “Static” component (does not account for timing)
 - ← Type of Logic Function (NOR vs. XOR)
 - ← Type of Logic Style (Static vs. Dynamic)
 - ← Signal Statistics
 - ← Inter-signal Correlations
- “Dynamic” or timing dependent component
 - ← Circuit Topology
 - ← Signal Statistics and Correlations

EECS141 Lecture #16 5



*Power
Revisited*

EECS141 Lecture #16 3

Type of Logic Function: NOR

Example: Static 2-input NOR Gate

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Assume signal probabilities
 $p_{A=1} = 1/2$
 $p_{B=1} = 1/2$

Then transition probability
 $p_{0 \rightarrow 1} = p_{Out=0} \times p_{Out=1}$
 $= 3/4 \times 1/4 = 3/16$

If inputs switch every cycle

$$\alpha_{0 \rightarrow 1} = 3/16$$

EECS141 Lecture #16 6

Type of Logic Function: NAND

Example: Static 2-input NAND Gate

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Assume signal probabilities

$$p_{A=1} = 1/2$$

$$p_{B=1} = 1/2$$

Then transition probability


$$p_{0 \rightarrow 1} = p_{Out=0} \times p_{Out=1}$$

$$= 3/4 \times 1/4 = 3/16$$

If inputs switch every cycle

$$\alpha_{0 \rightarrow 1} = 3/16$$

Problem: Reconvergent Fanout

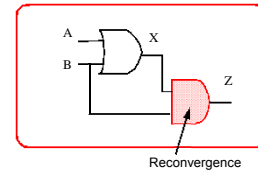

$$P(Z = 1) = P(B = 1) \cdot P(X = 1 | B=1)$$

Becomes complex and intractable fast

Type of Logic Function: XOR

Example: Static 2-input XOR Gate

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

Assume signal probabilities

$$p_{A=1} = 1/2$$

$$p_{B=1} = 1/2$$

Then transition probability


$$p_{0 \rightarrow 1} = p_{Out=0} \times p_{Out=1}$$

$$=$$

If inputs switch in every cycle


$$\alpha_{0 \rightarrow 1} =$$

Inter-Signal Correlations

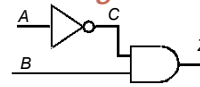

Logic without reconvergent fanout
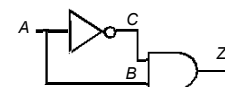
$$p_{0 \rightarrow 1} = (1 - p_A p_B) p_A p_B$$



Logic with reconvergent fanout

$$P(Z = 1) = p(C=1 | B=1) p(B=1)$$



$$p_{0 \rightarrow 1} = 0$$

- Need to use conditional probabilities to model inter-signal correlations
- CAD tools best for performing such analysis

Clock

- Always switches
- Often consumes 25-50% of total power
- Clock gating commonly employed

Glitching in Static CMOS

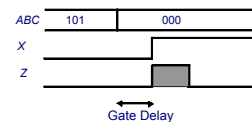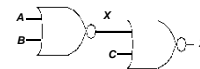

Also known as dynamic hazards

The result is correct, but there is extra power dissipated

Principles for Power Reduction

- Most important idea: reduce waste
- Examples:
 - Don't switch capacitors you don't need to
 - Clock gating, glitch elimination, logic re-structuring
 - Don't run circuits faster than needed
 - Power $\propto V_{DD}^2$ – can save a lot by reducing supply for circuits that don't need to be as fast
- Let's say we do a good job of that – then what?

EECS141

Lecture #16

13

Key Observation

- Define the Energy/Performance sensitivity of a parameter, for example:

$$S_{V_{DD}} = \frac{\partial \text{Energy} / \partial V_{DD}}{\partial \text{Perf} / \partial V_{DD}} \quad S_{V_T} = \frac{\partial \text{Energy} / \partial V_T}{\partial \text{Perf} / \partial V_T}$$


- At optimal point, sensitivities to all parameters should be the same (ignoring constraints)
 - Must equal slope of the Pareto optimal curve
 - Otherwise, could trade one parameter for another and end up with lower energy at same performance

EECS141

Lecture #16

16

Energy – Performance Space

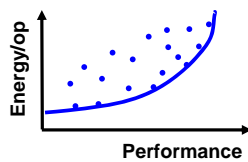

- Plot all possible designs on a 2-D plane
 - No matter what you do, can never get below/to the right of the solid line
- This line is called “Pareto Optimal Curve”
 - Usually (always) follows law of diminishing returns

EECS141

Lecture #16

14


Sensitivity Example

EECS141

Lecture #16

17

Optimization Perspective

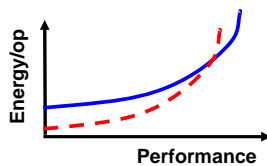

- Instead of metrics like EDP, this curve often provides information more directly
 - Ex1: What is minimum energy for XX performance?
 - Ex2: Over what range of performance is a new technique (dotted line) actually beneficial?

EECS141

Lecture #16

15

Sensitivity Example

EECS141

Lecture #16

18

Sensitivity Example

EECS141

Lecture #16

19

Next Lecture

- CMOS Scaling

EECS141

Lecture #16

20