



EE141-Fall 2012 Digital Integrated Circuits

Lecture 19 Dynamic Logic

Announcements

- Midterm 2: Thurs. Nov. 1st, 6:30-8:00pm
 - Includes all material up to and including Lecture 18
 - Exam starts at 6:30pm sharp
 - Review session: Tues. evening?

- Project phase 2 out next Thurs., due following Fri.

Class Material

- Last lecture
 - Ratioed and Pass-Transistor Logic
- Today's lecture
 - Dynamic logic
- Reading
 - Chapter 6



Dynamic Logic

Dynamic CMOS

- In **static** circuits, at every point in time (except when switching) the output is connected to either GND or V_{DD} via a low resistance path.
 - fan-in of n requires $2n$ (n N-type + n P-type) devices


- **Dynamic** circuits rely on the temporary storage of signal values on the capacitance of high impedance nodes.
 - only requires $n + 2$ ($n+1$ N-type + 1 P-type) transistors

EECS141

Lecture #19

5


Dynamic Gate

 

Two phase operation

Precharge (Clk = 0)

Evaluate (Clk = 1)

 

EECS141


Lecture #19

6

Conditions on Output


- Once the output of a dynamic gate is discharged, it cannot be charged again until the next precharge operation.
- Inputs to the gate can make **at most one rising** transition during evaluation.
- Output can be in the high impedance state during and after evaluation (PDN off), state is stored on C_L

LE of Dynamic Gates

 

$$C_{\text{gate}} =$$


$$LE =$$

 

$$C_{\text{gate}} =$$

$$LE =$$

Power Consumption of Dynamic Gates

 

Power only dissipated when previous Out = 0

Dynamic Power Consumption is Data Dependent

Dynamic 2-input NOR Gate

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Assume **signal probabilities**

$$P_{A=1} = 1/2$$

$$P_{B=1} = 1/2$$

Then **transition probability**

$$P_{0 \rightarrow 1} = P_{\text{out}=0} \times P_{\text{out}=1}$$

$$= 3/4 \times 1 = 3/4$$

Switching activity always **higher** in dynamic gates!

$$P_{0 \rightarrow 1} = P_{\text{out}=0}$$

Properties of Dynamic Gates


- Overall power dissipation usually **higher** than static CMOS
 - no static current path ever exists between V_{DD} and GND (including P_{sc})
 - no glitching
 - **higher transition probabilities**
 - **extra load on Clk**
- PDN starts to work as soon as the input signals exceed V_{Tn} , so V_M , V_{IH} and V_{IL} equal to V_{Tn}
 - low noise margin (NM_L)
- Needs a precharge/evaluate clock

EECS141

Lecture #19

11

 Issues in Dynamic Design 1: Charge Leakage



Leakage sources


Dominant component is subthreshold current

EECS141

Lecture #19



12

Solution to Charge Leakage

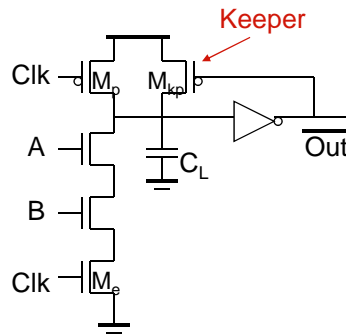


Same approach as level restorer for pass-transistor logic

Dynamic Gate VTC

  


Issues in Dynamic Design 2: Charge Sharing

 - Charge initially stored on C_L
 - C_A previously discharged




- When A rises, this charge is redistributed (shared) between C_L and C_A
- Makes Out drop below V_{DD}

Charge Sharing Example

 

Charge Sharing

 

- Two cases:
 - M_a stays on – complete charge share
 - M_a turns off – incomplete charge share

- Complete charge share:

- $Q_{Ca} = V_{Out} C_a$
 - $\Delta Q_{CL} = -V_{Out} C_a$


$$\rightarrow \Delta V_{Out} = -V_{DD} C_a / (C_a + C_L)$$

- Incomplete charge share:

- $Q_{Ca} = (V_{DD} - V_{TN}^*) C_a$
 - $\Delta Q_{CL} = -(V_{DD} - V_{TN}^*) C_a$

$$\rightarrow \Delta V_{Out} = -(V_{DD} - V_{TN}^*) C_a / C_L$$

Solution to Charge Sharing

 

- Keeper helps a lot
 - Can still get failures if Out drops below inverter V_{sw}
- Another option: precharge internal nodes
 - Increases power and area

Next Lecture

- Adders