




*EE141-Fall 2012
Digital Integrated
Circuits*

Lecture 22
Domino Logic

EECS141 Lecture #22 1



Domino Logic

EECS141 Lecture #22 4

Announcements

- Project phase 2 due Friday
 - Phase 3 out this Friday
- Homework #8 out next Tues., due following Tues.

EECS141 Lecture #22 2

Domino Logic

EECS141 Lecture #22 5

Class Material

- Last lecture
 - Multipliers
- Today's lecture
 - Domino logic
- Reading
 - Chapter 7

EECS141 Lecture #22 3

Why Named Domino?


Like falling dominos!

EECS141 Lecture #22 6

Properties of Domino Logic


- Only non-inverting logic can be implemented
- Very high speed
 - static inverter can be skewed, only L-H transition critical
 - Input capacitance reduced – smaller logical effort

Buffer "Average" LE

 

$LE_{\text{domo}} = \frac{2}{3}$
 $LE_{\text{static}} = \frac{5}{6}$
 $TLE = \frac{10}{18}$
 "Average" $LE = \sqrt{10/9} \approx \frac{3}{4}$

Domino Logic LE

 



$LE_{\text{domo}} =$
 $LE_{\text{static}} = 1$
 $TLE =$

$LE_{\text{domo}} =$
 $LE_{\text{static}} = 1$
 $TLE =$
 $LE_{\text{static}} = \frac{7}{3}$

Optimal EF/stage with Domino

- Domino buffers are faster than static CMOS inverters
- Is optimal EF/stage for a chain of domino gates still 4?


Domino Logic LE (skewed static gate)

  

$LE_{\text{domo}} =$
 $LE_{\text{static}} =$
 $TLE =$


Example

Designing with Domino Logic

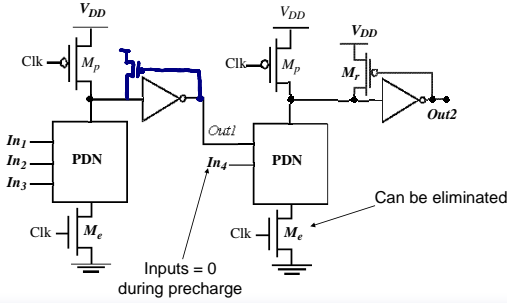


EECS141 Lecture #22 13

Footless Domino

 


EECS141 Lecture #22 16

Footless Domino

 


EECS141 Lecture #22 14

Differential (Dual Rail) Domino

 

EECS141 Lecture #22 17


Footless Domino

 

Can mitigate short-circuit current by alternating between footed and unfooted domino

EECS141 Lecture #22 15


np-CMOS

 

Only 0 → 1 transitions allowed at inputs of PDN
Only 1 → 0 transitions allowed at inputs of PUN

EECS141 Lecture #22 18

NORA Logic

 

Fast, but **EXTREMELY** sensitive to noise!

Next Lecture

□ Flops and Latches