

*EE141-Fall 2012
Digital Integrated
Circuits*

Lecture 23
Flops and Latches

EECS141 Lecture #23 1

Why Sequencing?


EECS141 Lecture #23 4

Announcements


- Homework #8 due next Tuesday
- Project Phase 3 part 1 due this Sun.
 - Poster: Wed. Nov. 28th
 - Final report: Mon. Dec. 3rd
- This Thurs. lecture will be “taped ahead”


EECS141 Lecture #23 2

Sequential Elements

 


Clk

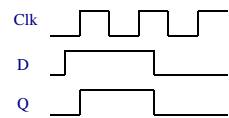

 


Clk

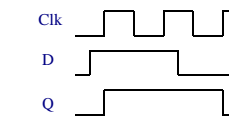

- Latch – level sensitive
 - Clk=0: “opaque”
 - Clk-1: “transparent”
- Flip-flop – edge triggered
 - Stores new data when Clk rises


EECS141 Lecture #23 5



*Sequential Elements:
Flops and Latches*


EECS141 Lecture #23 3

Timing Definitions - REVIEW

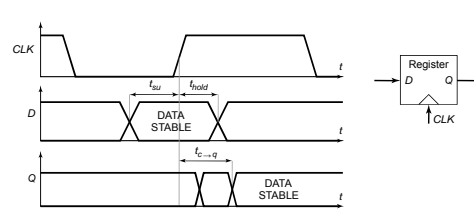


EECS141 Lecture #23 6

Storage Mechanisms

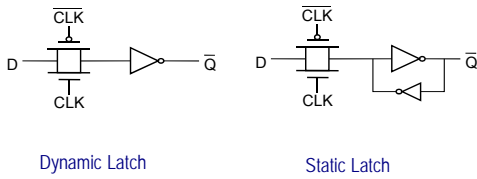


Master-Slave Register


Multiplexer-based latch pair

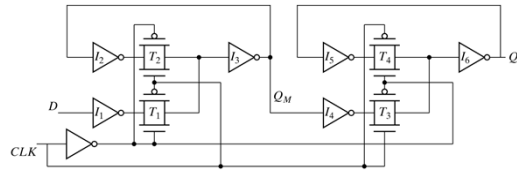


Writing Into a Static Latch

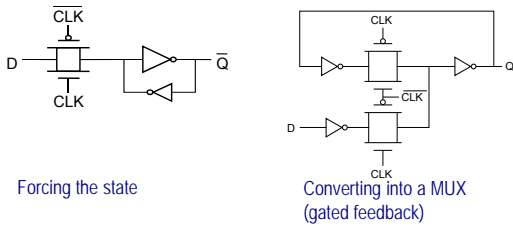

Register Timing: Clk-Q Delay

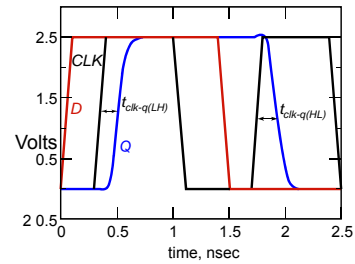


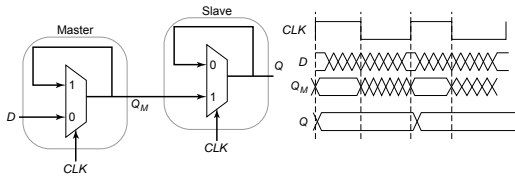Master-Slave Flip-Flop (Edge-Triggered Register)




Two opposite latches create edge-triggered behavior
Also called master-slave latch pair

Register Timing: Setup Time

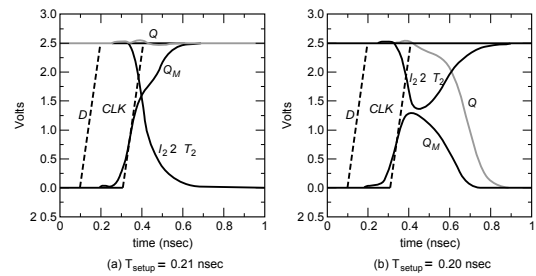

More Precise Setup Time

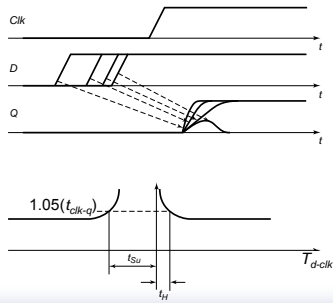


EECS141

Lecture #23

13

Setup-Hold Time Illustrations

Circuit before clock arrival (Setup-1 case)

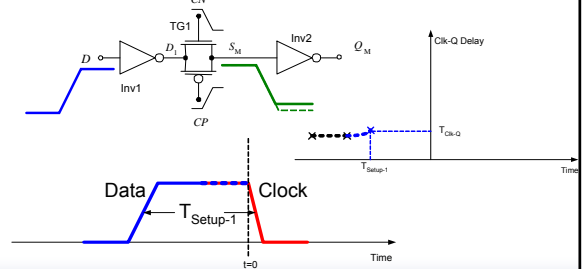


EECS141

Lecture #23

16

Setup-Hold Time Illustrations

Circuit before clock arrival (Setup-1 case)

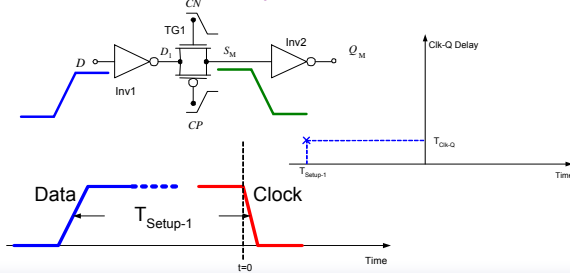


EECS141

Lecture #23

14

Setup-Hold Time Illustrations

Circuit before clock arrival (Setup-1 case)

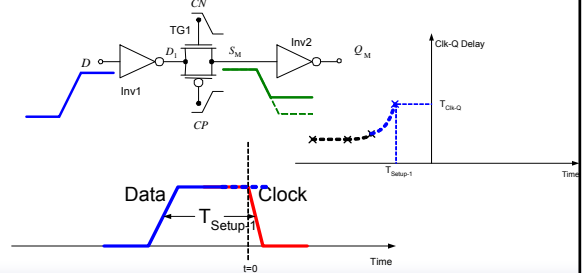


EECS141

Lecture #23

17

Setup-Hold Time Illustrations

Circuit before clock arrival (Setup-1 case)

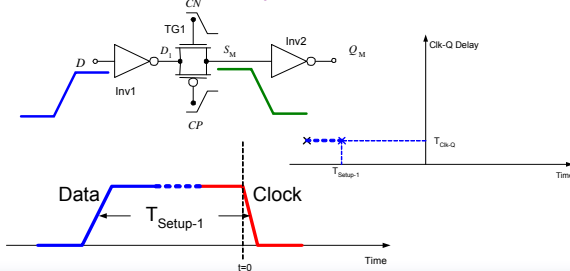


EECS141

Lecture #23

15

Setup-Hold Time Illustrations

Circuit before clock arrival (Setup-1 case)

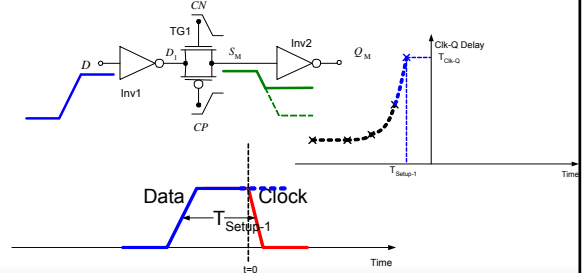

EECS141

Lecture #23

18

Setup-Hold Time Illustrations

Hold-1 case

Clock $t=0$ Data T_{Hold-1} Time

Clk-Q Delay T_{Clk-Q} T_{Rise-1} Time

EECS141 Lecture #23 19

Setup-Hold Time Illustrations

Hold-1 case

Clock $t=0$ Data T_{Hold-1} Time

Clk-Q Delay T_{Clk-Q} T_{Rise-1} Time

EECS141 Lecture #23 22

Setup-Hold Time Illustrations

Hold-1 case

Clock $t=0$ Data T_{Hold-1} Time

Clk-Q Delay T_{Clk-Q} T_{Rise-1} Time

EECS141 Lecture #23 20

Setup-Hold Time Illustrations

Hold-1 case

Clock $t=0$ Data T_{Hold-1} Time

Clk-Q Delay T_{Clk-Q} T_{Rise-1} Time

EECS141 Lecture #23 23

Setup-Hold Time Illustrations

Hold-1 case

Clock $t=0$ Data T_{Hold-1} Time

Clk-Q Delay T_{Clk-Q} T_{Rise-1} Time

EECS141 Lecture #23 21

Other Latches/Registers: C²MOS

Master Stage Slave Stage

*Usually includes feedback to staticize

EECS141 Lecture #23 24

C²MOS and Clock Overlap

EECS141 Lecture #23 25

Other Latches/Registers: Pulse-Triggered Latches

Master-Slave Latches

Pulse-Triggered Latch

EECS141 Lecture #23 28

Other Latches/Registers: TSPC

Positive latch
(transparent when CLK= 1)

Negative latch
(transparent when CLK= 0)

EECS141 Lecture #23 26

Why not route the pulse?

EECS141 Lecture #23 29

TSPC Operation

EECS141 Lecture #23 27

Next Lecture

- Timing

EECS141 Lecture #23 30