




*EE141-Fall 2012
Digital Integrated
Circuits*

Lecture 3
Switches, Inverters,
and Design Metrics

EECS141 Lecture #3 1

What is a Transistor?

An MOS Transistor ↔ A Switch!

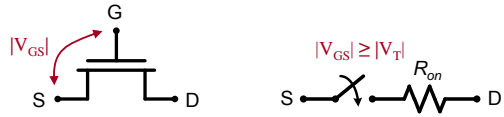


EECS141 Lecture #3 4

Administrative Stuff

- Discussions start tomorrow (Fri.)
- Labs start next week
 - Everyone should have an EECS instructional account
- Homework #1 is due today
- Homework #2 due next Thursday

EECS141 Lecture #3 2 ²

Switch Model of MOS Transistor

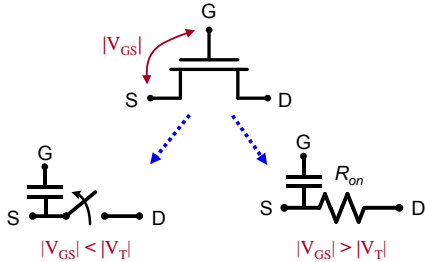

EECS141 Lecture #3 5


Class Material

- Last lecture
 - Basics of IC manufacturing, cost
- Today's lecture
 - Transistor as switches
 - Building an inverter
 - Design metrics

EECS141 Lecture #3 3

NMOS and PMOS

NMOS Transistor PMOS Transistor

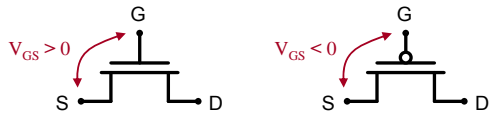

EECS141 Lecture #3 6

Building a CMOS inverter

Noise and Digital Systems

- Circuit needs to work despite “analog” noise
 - Digital gates can reject noise
 - This is actually how digital systems are defined
- Digital system is one where:
 - Discrete values mapped to analog levels and back
 - All the elements (gates) can reject noise
 - For “small” amounts of noise, output noise is less than input noise
 - Thus, for sufficiently “small” noise, the system acts as if it was noiseless

Design Metrics


- How to evaluate performance of a digital circuit (gate, block, ...)?
 - Cost
 - Reliability
 - Speed/Performance (delay, frequency)
 - Power

Noise Rejection

- To see if a gate rejects noise
 - Look at its DC voltage transfer characteristic (VTC)
 - See what happens when input is not exactly 1 or 0


□ Ideal digital gate:

 - Noise needs to be larger than $V_{DD}/2$ to have any effect on gate output









Reliability

 - The real world is analog
 - All physical quantities you deal with as a circuit designer are actually continuous
- Thus, even a “digital” signal can be noisy:




More Realistic VTC

 

  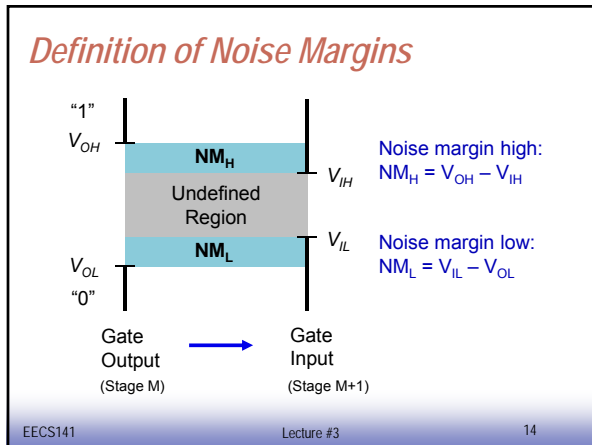 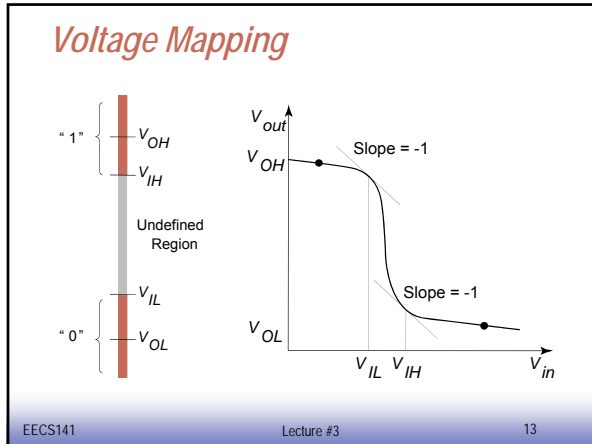

- ### Key Reliability Properties
- Absolute noise margin values are not the only things that matter
 - e.g., floating (high impedance) nodes are more easily disturbed than low impedance nodes (in terms of voltage)
 - Noise immunity (i.e., how well the gate suppresses noise sources) needs to be considered too
 - Summary of some key reliability metrics:
 - Noise transfer functions & margin (ideal: gain = ∞ , margin = $V_{dd}/2$)
 - Output impedance (ideal: $R_o = 0$)
 - Input impedance (ideal: $R_i = \infty$)
- EECS141 Lecture #3 18

 

Fanout of Four (FO4) Delay

- Want a way to characterize the delay of a circuit (roughly) independent of technology
- Most common metric:
 - Delay of an inverter driving four copies of itself (t_{FO4})

EECS141 Lecture #3 22

- ### Example: An Old-time Inverter
- $V_{OH} = 3.6V$
 - $V_{OL} = 0.4V$
 - $V_{IL} = 0.6V$
 - $V_{IH} = 2.3V$
 - $NM_H = V_{OH} - V_{IH} = 1.3V$
 - $NM_L = V_{IL} - V_{OL} = 0.2V$
- EECS141 Lecture #3 20


A First-Order RC Network

$$v_{out}(t) = (1 - e^{-t/\tau}) V$$

$$t_p = \ln(2) \tau = 0.69 RC$$

Important model – matches delay of an inverter

EECS141 Lecture #3 23

 

Power Dissipation

Instantaneous power:
 $p(t) = v(t)i(t) = V_{supply}i(t)$

Peak power:
 $P_{peak} = V_{supply}i_{peak}$

Average power:

$$P_{ave} = \frac{1}{T} \int_t^{t+T} p(t) dt = \frac{V_{supply}}{T} \int_t^{t+T} i_{supply}(t) dt$$

EECS141 Lecture #3 24

"Power-Delay" and Energy-Delay

- Want low power and low delay, so how about optimizing the product of the two?
 - So-called "Power-Delay Product"
- Power-Delay is by definition Energy
 - Optimizing this pushes you to go as slow as possible
- Alternative gate metric: Energy-Delay Product
 - $EDP = (P_{av} \cdot t_p) \cdot t_p = E \cdot t_p$

EECS141

Lecture #3

25

Energy Thought Experiment (1)


- Why doesn't R matter?

EECS141

Lecture #3

28

Energy in CMOS

 

- The voltage on C_L eventually settles to V_{DD}
- Thus, charge stored on the capacitor is $C_L V_{DD}$
 - This charge has to flow out of the power supply
- So, energy is just $Q \cdot V_{DD} = (C_L V_{DD}) \cdot V_{DD}$


EECS141

Lecture #3

26

Energy Thought Experiment (2)

- Where did the energy go?

 

$$E_{Vin} = C_L V_{in}^2$$


$$E_{CL} = (1/2) C_L V_{in}^2$$

EECS141

Lecture #3

29

Energy (the harder way)

 

$$E_{0 \rightarrow 1} = \int_0^T P_{DD}(t) dt = V_{DD} \int_0^T i_{DD}(t) dt = V_{DD} \int_0^{V_{DD}} C_L dv_{out} = C_L V_{DD}^2$$

$$E_C = \int_0^T P_C(t) dt = \int_0^T v_{out} i_L(t) dt = \int_0^{V_{DD}} C_L v_{out} dv_{out} = \frac{1}{2} C_L V_{DD}^2$$

EECS141

Lecture #3

27

Summary

- Understanding the design metrics that govern digital design is crucial
 - Cost
 - Robustness
 - Performance/speed
 - Power and energy dissipation

EECS141

Lecture #3

30

Next Lecture

- Detailed CMOS switch model
- Building gates with switches
- Design rules