



*EE141-Fall 2012  
Digital Integrated  
Circuits*

Lecture 6  
Inverter Delay Optimization


*Announcements*

- Homework #3 due Thursday
- Homework #4 due next Thursday

## *Class Material*

- Last lecture
  - Overview of Semiconductor Memory
- Today's lecture
  - Inverter Delay Optimization
- Reading (5.4, 5.5)


## *Inverter Chain*

 

- For some given  $C_L$ :
  - How many stages are needed to minimize delay?
  - How to size the inverters?
- Anyone want to guess the solution?
 
## *Careful about Optimization Problems*

- Get fastest delay if build one **very big** inverter
  - So big that delay is set only by self-loading



- Likely not the problem you're interested in
  - Someone has to drive this inverter...

## *Engineering Optimization Problems in General*

- Need to have a set of constraints
- Constraints key to:
  - Making the result useful
  - Making the problem have a 'clean' solution
- For sizing problem:
  - Need to constrain size of first inverter


## *Delay Optimization Problem #1*

- You are given:
  - A fixed number of inverters
  - The size of the first inverter
  - The size of the load that needs to be driven
  
- Your goal:
  - Minimize the delay of the inverter chain
  
- Need model for inverter delay vs. size
  - But first, a simple example...

## *Simple Example: Two Inverters*
 
## Inverter Delay

- Minimum length devices,  $L = 0.09\mu\text{m}$
- Assume that for  $W_p = 2W_n = 2W$ 
  - approximately equal resistances,  $R_N = R_p$
  - approx. equal rise and fall delays,  $t_{pHL} = t_{pLH}$




- Analyze as an RC network:

$$R_p = R_{sq,p} \left( \frac{L}{W_p} \right) \approx R_n = R_{sq,n} \left( \frac{L}{W_n} \right) = R_w$$

Delay:  $t_{pHL} = (\ln 2) R_n C_{tot} = t_{pLH} = (\ln 2) R_p C_{tot}$

Loading on the previous stage:  $C_{in} = 3WC_g$

## Inverter Delay

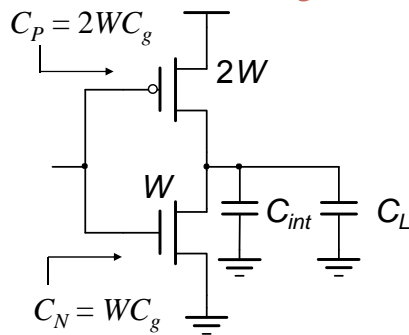

$$R_w = R_{sq,n} \left( \frac{L}{W} \right)$$

$$C_{int} = 3WC_d$$


$$C_{in} = 3WC_g$$

Replace  $\ln(2)$  with  $k$  (a constant):

$$\text{Delay} = kR_w C_{int} + kR_w C_L$$

$$\text{Delay} = kR_{sq,n} (L/W) (3WC_d) + kR_{sq,n} (L/W) C_L$$

## Inverter with Load

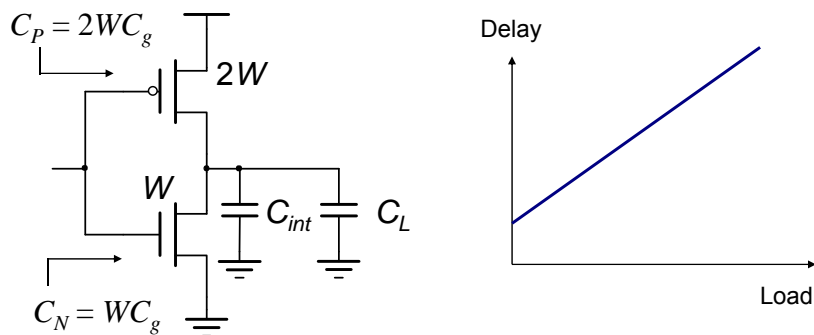

$$\begin{aligned} \text{Delay} &= kR_W C_{in} (C_{int}/C_{in} + C_L/C_{in}) \\ &= 3kLR_{sq,n} C_g [C_d/C_g + C_L/(3WC_g)] \\ &= \text{Delay (Internal)} + \text{Delay (Load)} \end{aligned}$$

EECS141

Lecture #6

11

## Delay Formula

$$\text{Delay} \sim R_W (C_{int} + C_L)$$

$$t_p = kR_W C_{in} (C_{int}/C_{in} + C_L/C_{in}) = t_{inv} (\gamma + f)$$

$$C_{int} = \gamma C_{in} \quad (\gamma \approx 1 \text{ for inverter})$$

$$f = C_L/C_{in} - \text{electrical fanout}$$

$$R_W = R_{sq}(L/W); \quad C_{in} = 3WC_g$$

$$t_{inv} = 3 \cdot \ln(2) \cdot L \cdot R_{sq} C_g$$


**$t_{inv}$  is independent of sizing of the gate!!!**

EECS141

Lecture #6

12

## Apply to Inverter Chain

 

$$t_p = t_{p1} + t_{p2} + \dots + t_{pN}$$

$$t_{pj} = t_{inv} \left( \gamma + \frac{C_{in,j+1}}{C_{in,j}} \right)$$

$$t_p = \sum_{j=1}^N t_{p,j} = t_{inv} \sum_{i=1}^N \left( \gamma + \frac{C_{in,j+1}}{C_{in,j}} \right), \quad C_{in,N+1} = C_L$$

## Optimal Tapering for Given N

- Delay equation has  $N-1$  unknowns,  $C_{in,2} \dots C_{in,N}$
- To minimize the delay, find  $N-1$  partial derivatives:

$$t_p = \dots + t_{inv} \frac{C_{in,j}}{C_{in,j-1}} + t_{inv} \frac{C_{in,j+1}}{C_{in,j}} + \dots$$

$$\frac{dt_p}{dC_{in,j}} = t_{inv} \frac{1}{C_{in,j-1}} - t_{inv} \frac{C_{in,j+1}}{C_{in,j}^2} = 0$$

## Optimal Tapering for Given N (cont'd)

- Result: every stage has equal fanout:

$$\frac{C_{in,j}}{C_{in,j-1}} = \frac{C_{in,j+1}}{C_{in,j}}$$

- In other words, size of each stage is geometric mean of two neighbors:

$$C_{in,j} = \sqrt{C_{in,j-1} C_{in,j+1}}$$

- Equal fanout  $\rightarrow$  every stage will have same delay

## Optimum Delay and Number of Stages

- When each stage has same fanout  $f$ :

$$f^N = F = C_L / C_{in,1}$$

- Effective fanout of each stage:


$$f = \sqrt[N]{F}$$

- Minimum path delay:

$$t_p = N t_{inv} \left( \gamma + \sqrt[N]{F} \right)$$



## Example

 

$C_L/C_1$  has to be evenly distributed across  $N = 3$  stages:

$$f = \sqrt[3]{8} = 2$$

## Delay Optimization Problem #2

- You are given:
  - The size of the first inverter
  - The size of the load that needs to be driven
- Your goal:
  - Minimize delay by finding optimal number and sizes of gates
- So, need to find  $N$  that minimizes:

$$t_p = N t_{inv} \left( \gamma + \sqrt[N]{C_L / C_{in}} \right)$$

## Intuitive Example

## Solving the Optimization

- Rewrite  $N$  in terms of fanout/stage  $f$ :

$$f^N = C_L/C_{in} \rightarrow N = \frac{\ln(C_L/C_{in})}{\ln f}$$

$$t_p = N t_{inv} \left( (C_L/C_{in})^{1/N} + \gamma \right) = t_{inv} \ln(C_L/C_{in}) \left( \frac{f + \gamma}{\ln f} \right)$$


$$\frac{\partial t_p}{\partial f} = t_{inv} \ln(C_L/C_{in}) \cdot \frac{\ln f - 1 - \gamma/f}{\ln^2 f} = 0$$

$$f = \exp(1 + \gamma/f) \quad \text{For } \gamma = 0, f = e, N = \ln(C_L/C_{in})$$

## Optimum Effective Fanout $f$


- Optimum  $f$  for given process defined by  $\gamma$

$$f = \exp(1 + \gamma/f)$$

 

- Intuition: why does  $f$  go up with  $\gamma$ ?

## In Practice: Plot of Total Delay

 

- Curves very flat for  $f > 2$ 
  - Simplest/most common choice:  $f = 4$

## Normalized Delay As a Function of F





$$t_p = N t_{inv} (\gamma + \sqrt[N]{F}), \quad F = C_L / C_{in}$$

F	Unbuffered	Two Stage	Inverter Chain
10	11	8.3	8.3
100	101	22	16.5
1000	1001	65	24.8
10,000	10,001	202	33.1


( $\gamma = 1$ )

Textbook: page 210

## Buffer Design

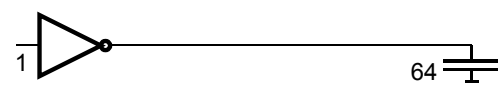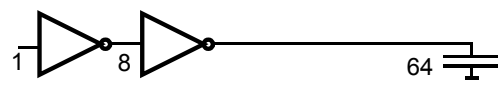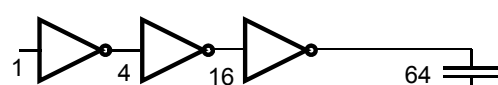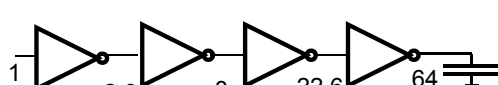	N	f	t <sub>p</sub>
	1	64	65
	2	8	18
	3	4	15
	4	2.8	15.3

## What About Energy (and Area)?

 

Ignoring diffusion capacitance:

$$\begin{aligned}
 C_{tot} &= C_{in} + f \cdot C_{in} + \dots + f^N \cdot C_{in} \\
 &= C_{in} \cdot (1 + f + \dots + f^N) \\
 &= C_{in} + C_{in} \cdot f^N + C_{in} \cdot f \cdot (1 + f + \dots + f^{N-1})
 \end{aligned}$$


2)

**Overhead !!!**  $f(f^{N-1}-1) / (f-1)$

**Example ( $\gamma=0$ ):**  $C_L = 20\text{pF}$ ;  $C_i = 50\text{fF} \rightarrow N = 6$   
 Fixed:  $20\text{pF}$   
 Overhead:  **$11.66\text{pF !!!}$**

## Example Overhead Numbers

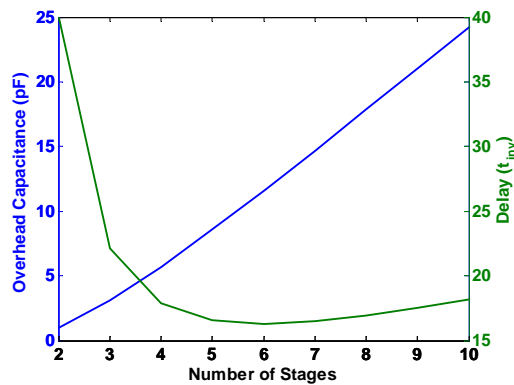**Example:**  $C_L = 20\text{pF}$ ;  $C_{in} = 50\text{fF}$



## *Example Problem*

EECS141

Lecture #6

27

## *Next Lecture*

- Gate Delay
- Logical Effort

EECS141

Lecture #6

28