

*EE141-Fall 2012
Digital Integrated
Circuits*

Lecture 7
Gate Delay and
Logical Effort

Announcements

- Homework #3 due today

- Homework #4 due next Thursday

Class Material

- Last lecture
 - Inverter delay optimization
- Today's lecture
 - Gate delay and logical effort
- Reading (Chapter 6)


EECS141

Lecture #7

3

Complex Gate Delay

- Use RC model to estimate delay:

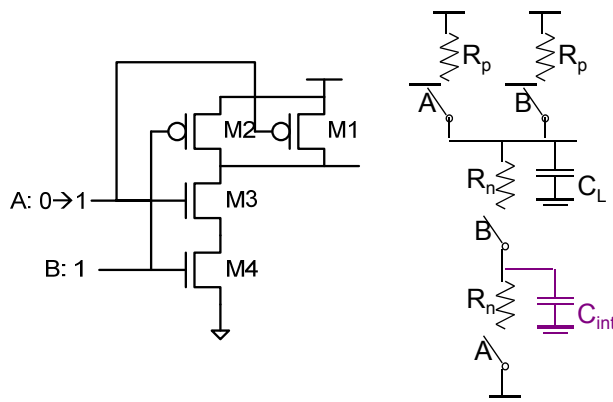


EECS141

Lecture #7

4

Complex Gate Delay (2)

□ Now what is the delay?

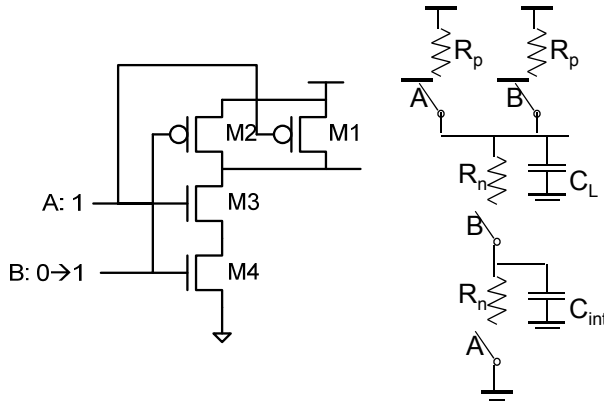


EECS141

Lecture #7

5

Elmore Delay

 


- “Elmore delay”: approximation for delay of arbitrary (complex) RC circuits
- To find “Elmore time constant”:
 - For each capacitor, draw path of current from cap to input
 - Multiply C by sum of R 's on current path that are common with path from V_{in} to V_{out}
 - Add up RC products from all capacitors

EECS141

Lecture #7


6

Elmore Delay (Formal Method)

 


- Set V_{in} to (incremental) ground
- Apply current I across C , measure V_{out}
- Calculate $R_{eff} = V_{out}/I$
- Time constant due to that C is $R_{eff} * C$

Simplified Model: Elmore Delay

 

$$\tau_{Elmore} = R_1 C_1 + (R_1 + R_2) C_2 + (R_1 + R_2 + R_3) C_3$$


Another Elmore Delay Example

 


$$\tau_{Elmore} =$$

Another Example Gate


Gate Sizing

 

Sizing Example

 




$$OUT = D + A \cdot (B + C)$$

 

Logical Effort

   
Question #1

- All of these are decoders
 - Which one is “best”?



 
Question #2

- Is it better to drive a big capacitive load directly with the NAND gate, or after some buffering?



- Method to answer both of these questions:
 - Logical effort
 - Extension of buffer sizing problem

Buffer Chain Review

 

$$Delay = t_{inv} \sum_{i=1}^N (\gamma + f_i)$$

$$f_i = C_{i+1}/C_i$$


For given N : $C_{i+1}/C_i = C_i/C_{i-1}$
 To find N : $C_{i+1}/C_i \sim 4$

Delay of NAND Gate

$$C_{dnand} = 6C_D$$

$$C_{gnand} = 4C_G = (4/3) C_{ginv}$$

$$C_D/C_G = \gamma$$

 

$$t_{pNAND} = kR_W(C_{int} + C_L)$$

$$= k(R_{sq,n} * L/W)(WC_{dnand} + C_L)$$

$$= k(R_{sq,n} * L * C_{gnand})(C_{dnand} / C_{gnand} + C_L / (WC_{gnand}))$$

$$= k(R_{sq,n} * L * 4 * C_g)(3/2 * \gamma + C_L / (WC_{gnand}))$$

$$= (4/3) t_{inv} (3/2 \gamma + f)$$

EECS141

Lecture #7


17

Delay of NOR Gate

$$C_{dnor} = 6C_D$$

$$C_{gnor} = 5C_G = (5/3) C_{ginv}$$

$$C_D/C_G = \gamma$$

 

$$t_{pNAND} = kR(C_{int} + C_L)$$

$$= k(R_{sq,n} * L/W)(WC_{dnor} + C_L)$$

$$= k(R_{sq,n} * L * C_{gnor})(C_{dnor} / C_{gnor} + C_L / (WC_{gnor}))$$

$$= k(R_{sq,n} * L * 5 * C_g)(6/5 * \gamma + C_L / (WC_{gnor}))$$


$$= (5/3) t_{inv} (6/5 \gamma + f)$$

EECS141

Lecture #7

18

Sizing a Chain

 


$$t_{p,tot} = t_{inv}[(\gamma + C_{nd}/C_{inv}) + 4/3*(3/2*\gamma + C_{nr}/C_{nd}) + 5/3*(6/5*\gamma + C_L/C_{nr})]$$

$$= t_{inv}[(\gamma + C_{nd}/C_{inv}) + (2\gamma + (4/3)*C_{nr}/C_{nd}) + (2\gamma + (5/3)*C_L/C_{nr})]$$

□ You already know how to solve this!

- NAND and NOR are just like inverters
- Except that their fanout looks larger – i.e., get more delay than an inverter for same fanout

Logical Effort

 

$$t_{p,tot} = t_{inv}[(\gamma + C_{nd}/C_{inv}) + 4/3*(3/2*\gamma + C_{nr}/C_{nd}) + 5/3*(6/5*\gamma + C_L/C_{nr})]$$

$$= t_{inv}[(\gamma + C_{nd}/C_{inv}) + (2\gamma + (4/3)*C_{nr}/C_{nd}) + (2\gamma + (5/3)*C_L/C_{nr})]$$

p_{gate}

parasitic delay $\neq f(W)$

LE

logical effort $\neq f(W)$

f

electrical fanout

$$t_{pgate} = t_{inv} (p_{gate} + LE \cdot f)$$

Finding Logical Effort of a Gate

- Inverter has the smallest logical effort and intrinsic delay of all static CMOS gates
 - So normalize everything to inverter
- Logical effort LE is defined as:
 - $(R_{eq,gate} C_{in,gate}) / (R_{eq,inv} C_{in,inv})$
 - Easiest way to calculate (usually):
 - Size gate to deliver same current as an inverter, take ratio of gate input capacitance to inverter capacitance
- LE increases with gate complexity


EECS141

Lecture #7

21

Finding Logical Effort of a Gate

Calculating LE by sizing for same drive strength:

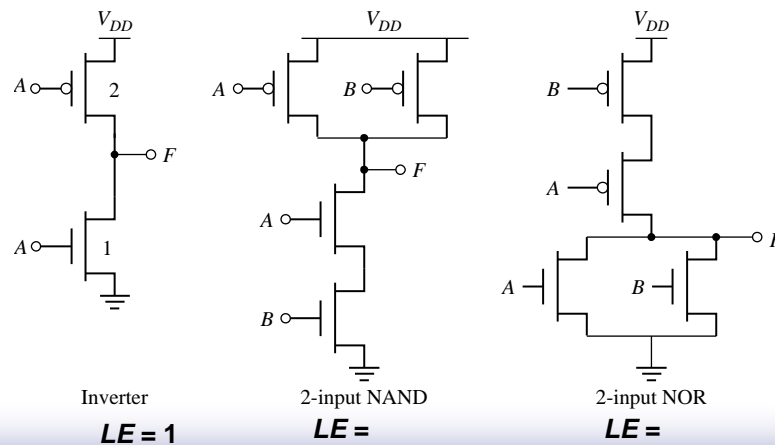

EECS141

Lecture #7

22


Gate Sizing Convention

- Need to set a convention:
 - What does a gate of size '2' mean?
- For an inverter it is clear:
 - $C_{inv} = 2, R_{inv} = 1/2$
- For a gate, two possibilities:
 - $C_{gate} = 2C_{inv} \rightarrow R_{gate} = (LE/2)*R_{inv}$
 - $R_{gate} = R_{inv}/2 \rightarrow C_{gate} = (2*LE)*C_{inv}$
- In my notes, **size** $\equiv C_{gate}/C_{inv}$
 - Size 2 gate has twice the input capacitance of a unit inverter


Adding Branching

Branching effort:
 
$$b = \frac{C_{L,on-path} + C_{L,off-path}}{C_{L,on-path}}$$



Chain of Arbitrary Gates

 

Effective fanout: $EF_i = LE_i f_i$

Path electrical fanout: $F = C_{out}/C_{in}$

Path logical effort: $\Pi LE = LE_1 LE_2 \dots LE_N$

Branching effort: $\Pi B = b_1 b_2 \dots b_N$

Path effort: $PE = \Pi LE \Pi B F$

Path delay $D = \sum d_i = \sum p_i + \sum EF_i$

Optimum EF/Stage

- Just like buffer chain, but use (PE, EF) instead of (F, f):

$$EF^N = PE$$

$$EF = \sqrt[N]{PE}$$

Effective fanouts: $LE_1 f_1 = LE_2 f_2 = \dots = LE_N f_N$

Minimum path delay

$$\hat{D} = \sum_{i=1}^N (LE_i f_i + p_i) = N \cdot PE^{1/N} + \sum_{i=1}^N p_i$$

Optimal Number of Stages


For a given load,
and given input capacitance of the first gate
Find optimal number of stages and optimal sizing

$$D = N \cdot PE^{1/N} + \sum p_i$$

Remember: we can always add inverters to the end of the chain

The 'best effective fanout' $EF = PE^{1/\hat{N}}$ is still around 4
(3.6 with $\gamma=1$)

Example: Optimize Path

 

Electrical fanout, $F =$

$\prod LE =$

$PE =$


$EF/\text{stage} =$

$a =$

$b =$

$c =$

Example: Optimize Path

 

$LE = 1$ $LE = 5/3$ $LE = 5/3$ $LE = 1$
 $f = a$ $f = b/a$ $f = c/b$ $f = 5/c$

Electrical fanout, $F = 5$
 $\Pi LE = 1 \cdot (5/3) \cdot (5/3) \cdot 1 = (25/9)$
 $PE = (\Pi LE) \cdot F = (125/9)$
 $EF/stage = (125/9)^{(1/4)} = 1.93$
 $a = 1.93$
 $b = 2.23$
 $c = 2.59$

$5/c = 1.93$
 $(5/3)c/b = 1.93$
 $(5/3)b/a = 1.93$

Method of Logical Effort

- Compute the path effort: $PE = (\Pi LE)BF$
- Find the best number of stages $N \sim \log_4 PE$
- Compute the effective fanout/stage $EF = PE^{1/N}$
- Sketch the path with this number of stages
- Work either from either end, find sizes:
 $C_{in} = C_{out} * LE/EF$

Reference: Sutherland, Sproull, Harris, "Logical Effort, Morgan-Kaufmann 1999.

Next Lecture

- Applying logical effort to a decoder