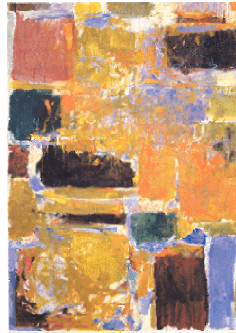


EE141-Spring 2006 Digital Integrated Circuits

Lecture 25
Clock Distribution
Power Distribution

EECS141



Clock Distribution

EECS141


Administrative Stuff

- Homework #9 due this Thursday
- Visit to Intel, April 21
 - Signup sheet
 - Friday lab - project ph. 4 starts after we get back
- Project phase 4
 - Posted
 - In lab April 21-April 27
- Hardware lab this week
 - Friday section on April 28

EECS141

Clock Distribution

H-tree

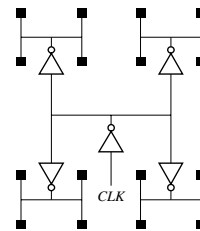

Clock is distributed in a tree-like fashion


EECS141

Class Material

- Last lecture
 - Timing
- Today's lecture
 - Clock distribution
 - Power distribution
- Reading
 - Chapter 10, 9 (pp. 453-462, 469-475, 508-515)

EECS141


More realistic H-tree

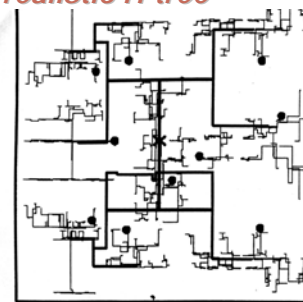

[Restle98]


EECS141

The Grid System

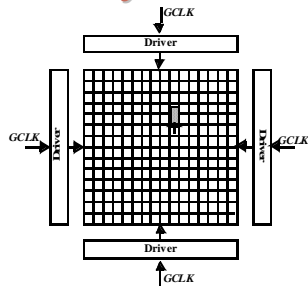

- No rc-matching
- Large power

EECS141

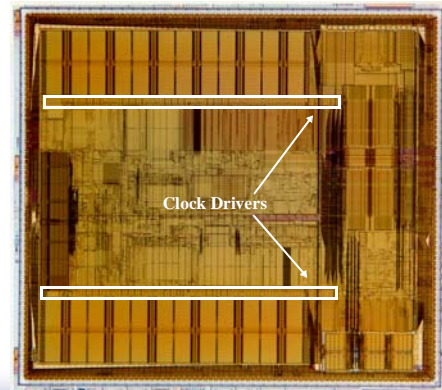

EECS141

Example: DEC Alpha 21164

Clock Frequency: 300 MHz - 9.3 Million Transistors

Total Clock Load: 3.75 nF


Power in Clock Distribution network : 20 W (out of 50)

Uses Two Level Clock Distribution:

- Single 6-stage driver at center of chip
 - Secondary buffers drive left and right side clock grid in Metal3 and Metal4
- Total driver size: 58 cm!**


EECS141

Clock Skew in Alpha Processor

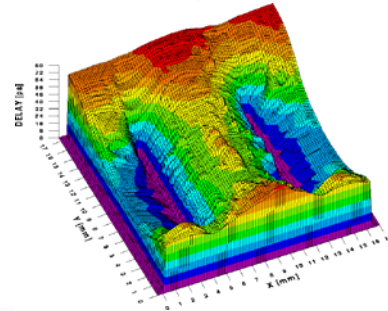


EECS141

21164 Clocking

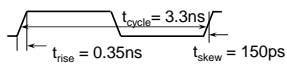

Clock waveform

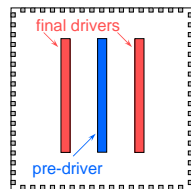


Location of clock driver on die


- 2 phase single wire clock, distributed globally
- 2 distributed driver channels
 - Reduced RC delay/skew
 - Improved thermal distribution
 - 3.75nF clock load
 - 58 cm final driver width
- Local inverters for latching
- Conditional clocks in caches to reduce power
- More complex race checking
- Device variation

EECS141

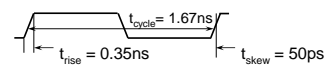EV6 (Alpha 21264) Clocking 600 MHz - 0.35 micron CMOS




Global clock waveform

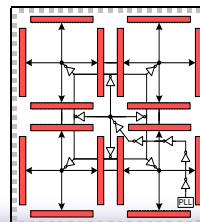

- 2 Phase, with multiple conditional buffered clocks
 - 2.8 nF clock load
 - 40 cm final driver width
- Local clocks can be gated "off" to save power
- Reduced load/skew
- Reduced thermal issues
- Multiple clocks complicate race checking

EECS141

21264 Clocking

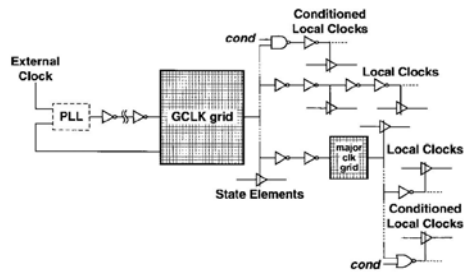

EECS141


Clock Animations

□ By Phillip Restle (IBM)

<http://www.research.ibm.com/people/r/restle/Animations/DAC01top.html>

EECS141

EV6 Clock Results

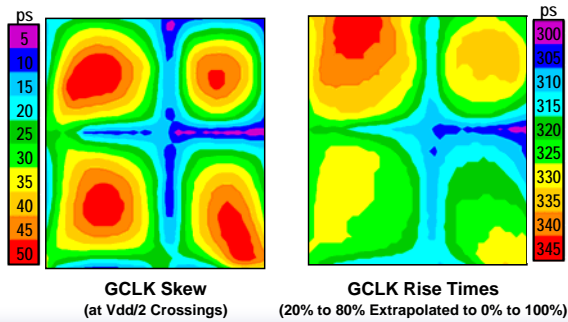

EECS141




I/O Design

EECS141

EV7 Clock Hierarchy

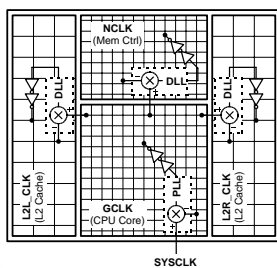
Active Skew Management and Multiple Clock Domains



- + widely dispersed drivers
- + DLLs compensate static and low-frequency variation
- + divides design and verification effort
- DLL design and verification is added work
- + tailored clocks

EECS141

Bonding Pad Design

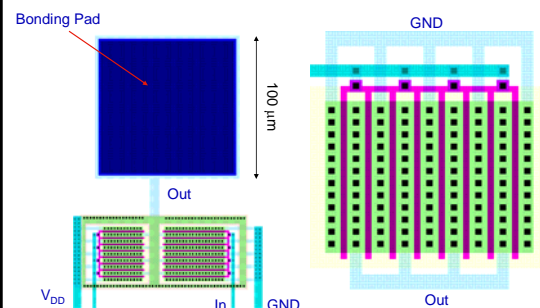

EECS141


ESD Protection

- When a chip is connected to a board, there is unknown (potentially large) static voltage difference
- Equalizing potentials requires (large) charge flow through the pads
- Diodes sink this charge into the substrate – need guard rings to pick it up.


EECS141

Pad Frame

Layout

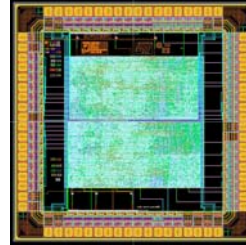


Die Photo

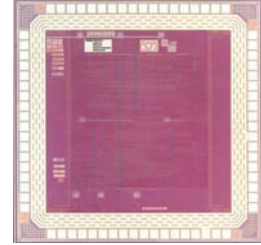

EECS141


ESD Protection

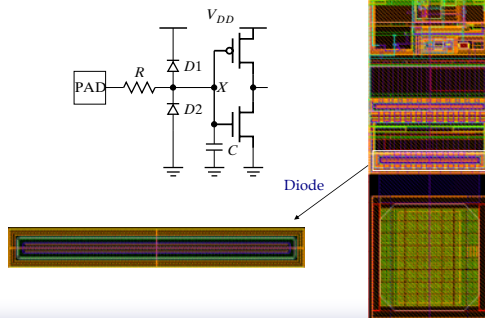

EECS141


Chip Packaging

- An alternative is 'flip-chip':
 - Pads are distributed around the chip
 - The soldering balls are placed on pads
 - The chip is 'flipped' onto the package
 - Can have many more pads

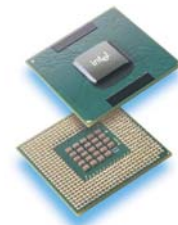

EECS141

Chip Packaging

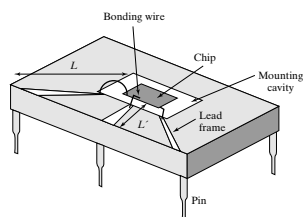

- Bond wires (~25μm) are used to connect the package to the chip
- Pads are arranged in a frame around the chip
- Pads are relatively large (~100μm in 0.25μm technology), with large pitch (100μm)
- Many chips areas are 'pad limited'

EECS141



Power Distribution

EECS141

Impact of Resistance

- We have already learned how to drive RC interconnect
- Impact of resistance is commonly seen in power supply distribution:
 - IR drop
 - Voltage variations
- Power supply is distributed to minimize the IR drop and the change in current due to switching of gates


EECS141

Power Distribution

- Low-level distribution is in Metal 1
- Power has to be 'strapped' in higher layers of metal.
- The spacing is set by IR drop, electromigration, inductive effects
- Always use multiple contacts on straps


EECS141

RI Introduced Noise

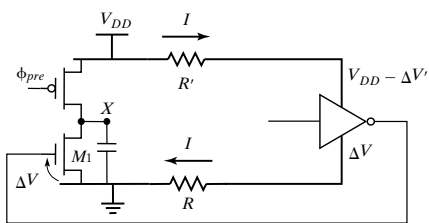

EECS141


Power and Ground Distribution

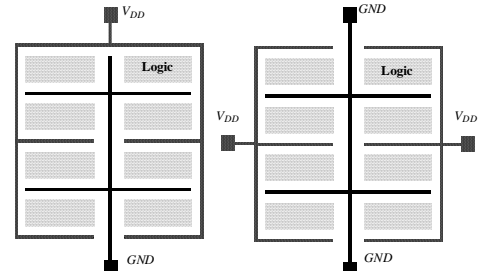

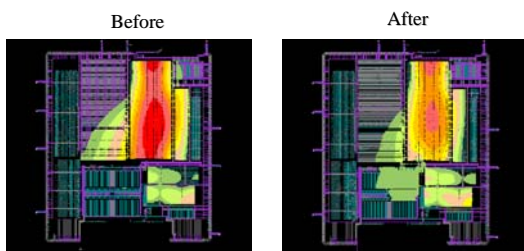(a) Finger-shaped network (b) Network with multiple supply pins

EECS141

Resistance and the Power Distribution Problem




- Requires fast and accurate peak current prediction
- Heavily influenced by packaging technology

EECS141

Source: Cadence

3 Metal Layer Approach (EV4)

3rd "coarse and thick" metal layer added to the technology for EV4 design
 Power supplied from two sides of the die via 3rd metal layer
 2nd metal layer used to form power grid
 90% of 3rd metal layer used for power/clock routing

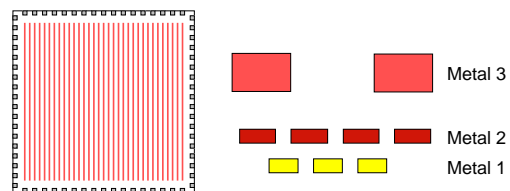

EECS141

Courtesy Compaq


4 Metal Layers Approach (EV5)

4th "coarse and thick" metal layer added to the technology for EV5 design

Power supplied from four sides of the die

Grid strapping done all in coarse metal

90% of 3rd and 4th metals used for power/clock routing

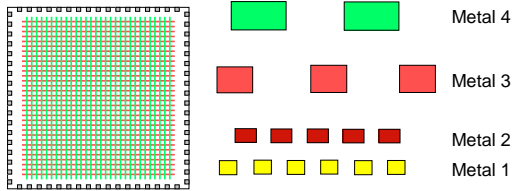


EECS141

Courtesy Compaq

Decoupling Capacitors

- Under the die

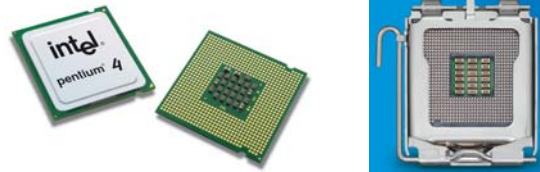

EECS141


6 Metal Layer Approach - EV6

2 reference plane metal layers added to the technology for EV6 design

Solid planes dedicated to Vdd/Vss

Significantly lowers resistance of grid

Lowers on-chip inductance

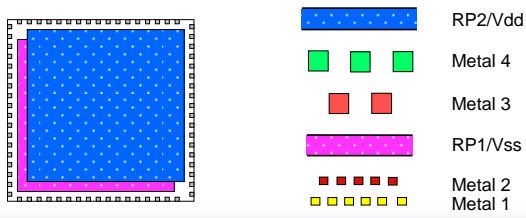

EECS141


Courtesy Compaq

Next Lecture

- Adder design

EECS141

Decoupling Capacitors

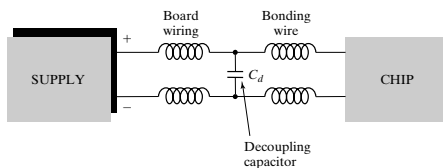

Decoupling capacitors are added:

- On the board (right under the supply pins)
- On the chip (under the supply straps, near large buffers)

EECS141