

EE141- Spring 2003

Lecture 4

Design Rules
CMOS Inverter
MOS Transistor Model



EE141

Today's lecture

- Design Rules
- The CMOS inverter at a glance
- An MOS transistor model for manual analysis

EE141

Important!

- Labs start next week
- You must show up in one of the lab sessions next week
- If you don't show up you will be dropped from the class
 - » Unless you let me know that you still want to be in the class
- Homework 2 will be posted later today. Due next Thursday, February 6.

EE141


Design Rules

Jan M. Rabaey



EE141

3D Perspective

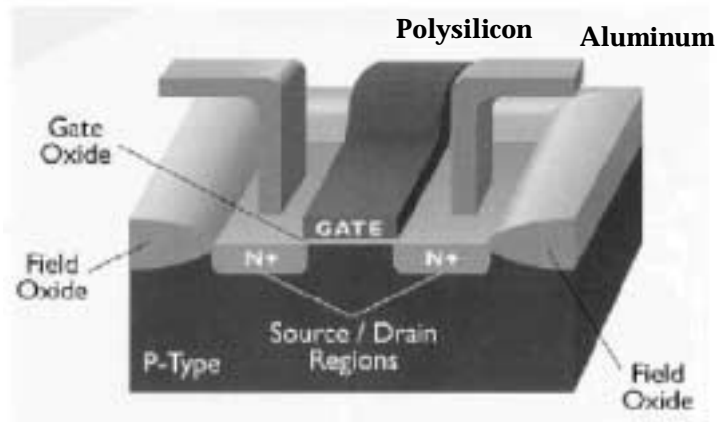

 








EE141

Design Rules

 - Interface between designer and process engineer
- Guidelines for constructing process masks
- Unit dimension: Minimum line width
 - » scalable design rules: lambda parameter
 - » absolute dimensions (micron rules)














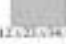





EE141

CMOS Process Layers

Layer	Color	Representation
Well (p,n)	Yellow	
Active Area (n+,p+)	Green	
Select (p+,n+)	Green	
Polysilicon	Red	
Metal1	Blue	
Metal2	Magenta	
Contact To Poly	Black	
Contact To Diffusion	Black	
Via	Black	


EE141

Layers in 0.25 μm CMOS process

Layer Description	Representation				
metal	 m1	 m2	 m3	 m4	 m5
well	 w0				
polysilicon	 poly				
contacts & vias	 c1	 c2, c3, c4, c5	 c3	 c4	 c5
active areas and FEFs	 a1	 a2	 a3	 a4	
select	 s1	 s2	 s3		


EE141

Intra-Layer Design Rules

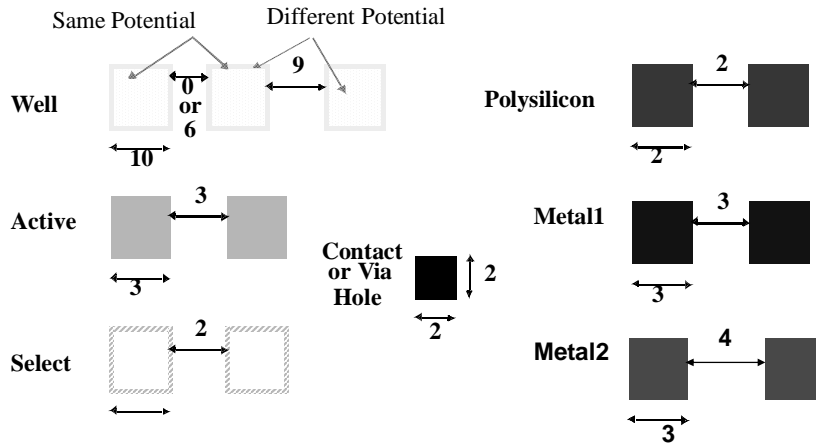


EE141

Transistor Layout

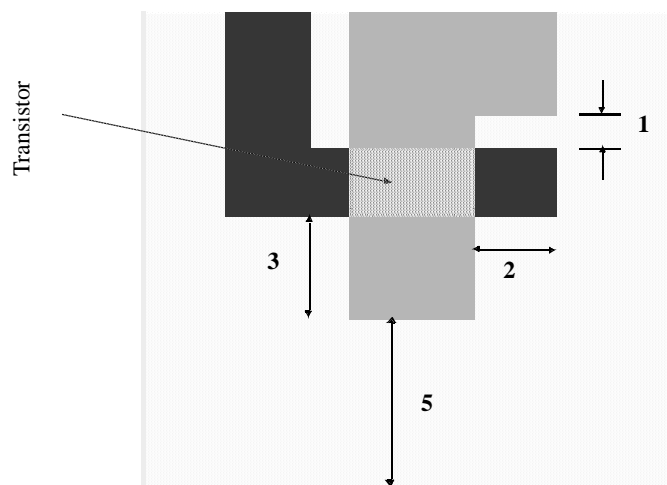


EE141

Vias and Contacts

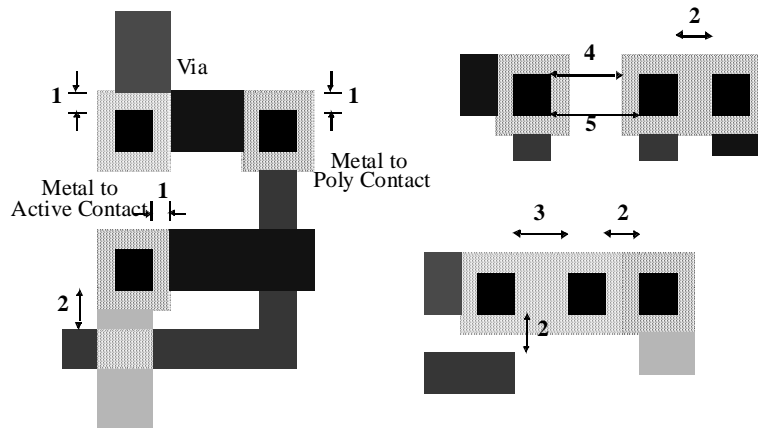


EE141

Select Layer

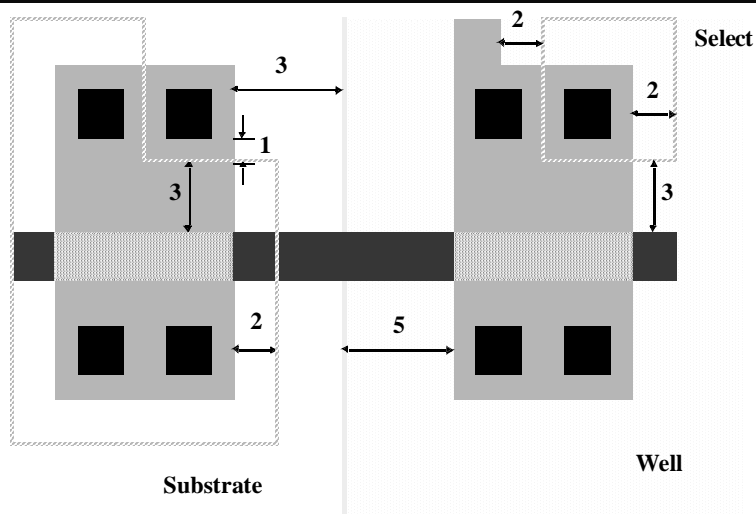


EE141

CMOS Inverter Layout

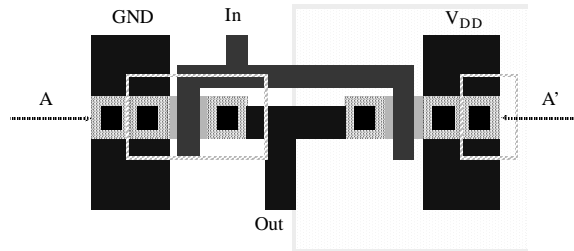


(a) Layout

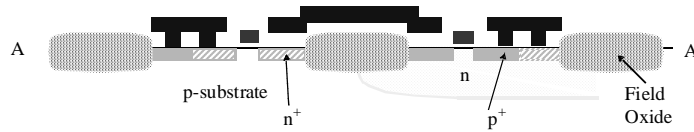

(b) Cross-Section along A-A'


EE141

Layout Editor

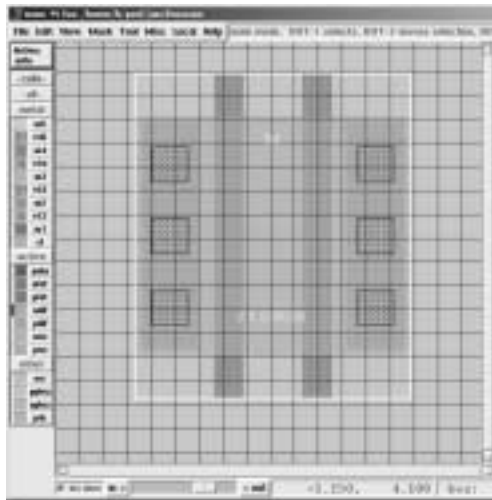


EE141

Design Rule Checker

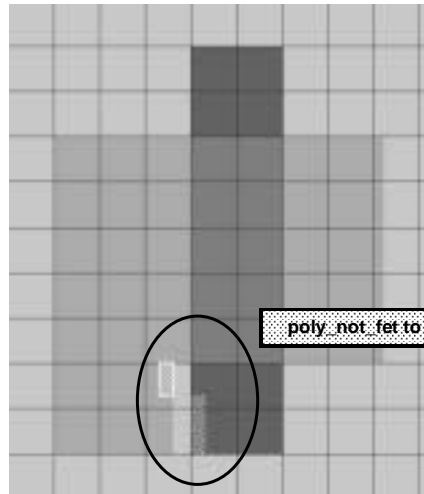

EE141

Sticks Diagram

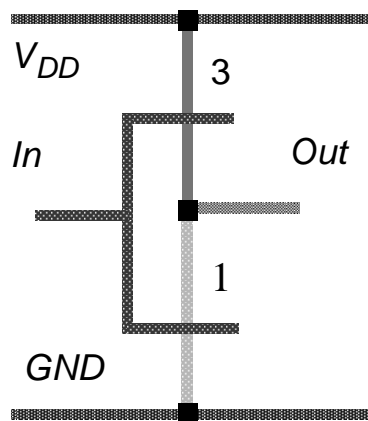


- Dimensionless layout entities
- Only topology is important
- Final layout generated by “compaction” program

Stick diagram of inverter

EE141

CMOS Inverter MOS Transistor



Jan M. Rabaey

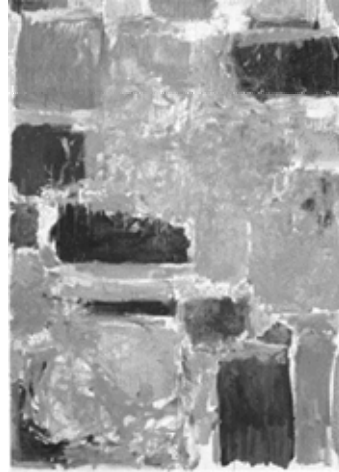

EE141

What is a Transistor?


A MOS Transistor \longleftrightarrow A Switch!

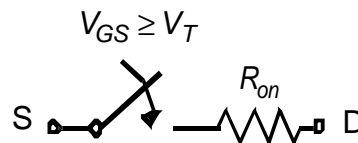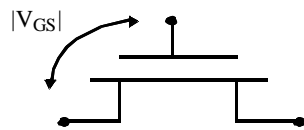


EE141

NMOS and PMOS

NMOS Transistor

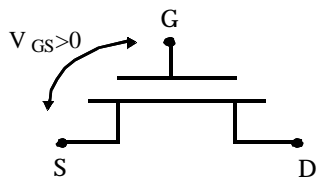


PMOS Transistor

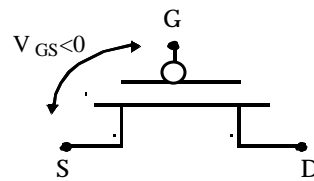



EE141

The CMOS Inverter: A First Glance

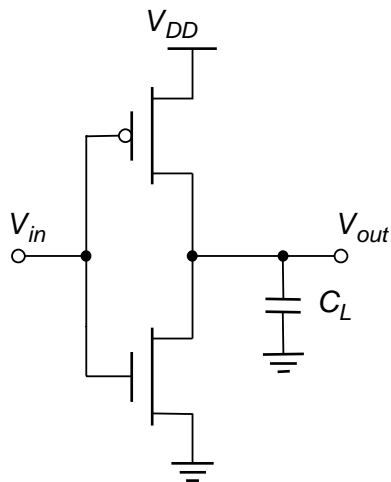

EE141

CMOS Inverter

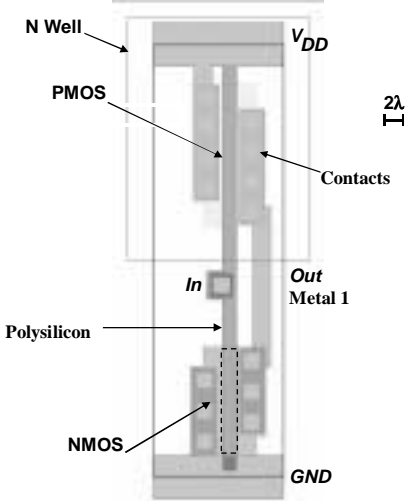
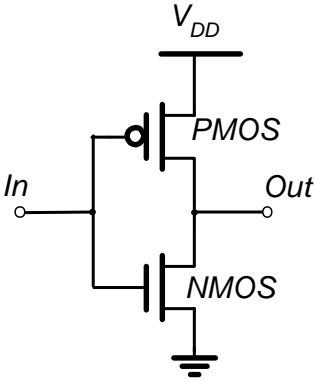


EE141

Two Inverters


Share power and ground

Abut cells

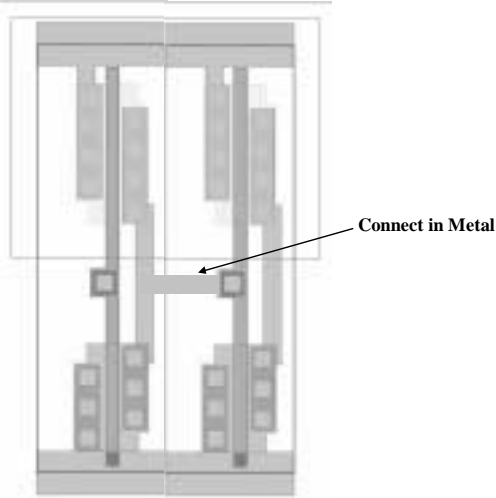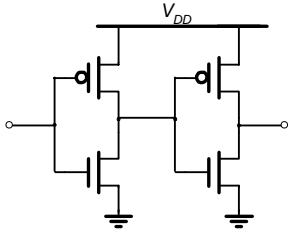


EE141

Switch Model of CMOS Transistor

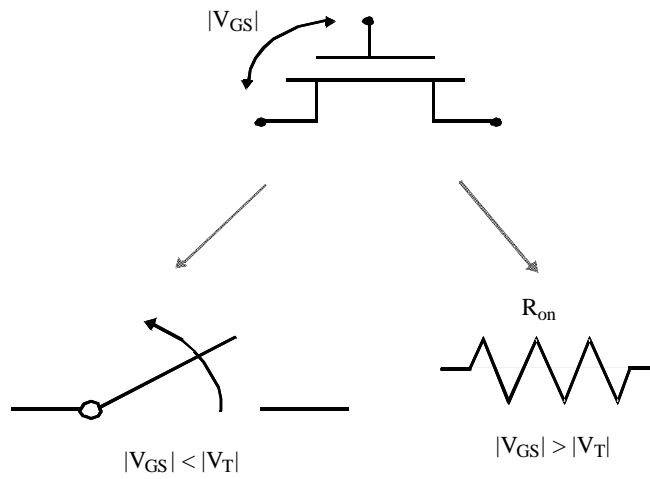

EE141


CMOS Inverter First-Order DC Analysis

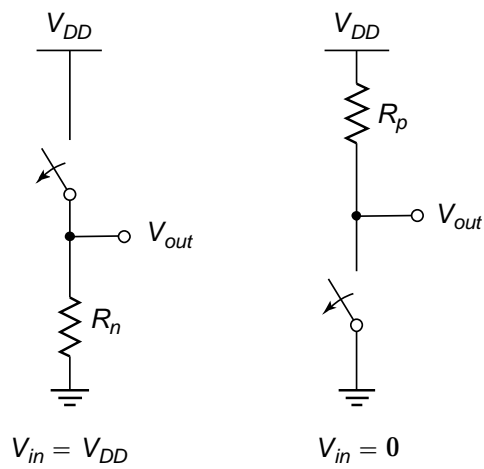

$$\begin{aligned}
 V_{OL} &= 0 \\
 V_{OH} &= V_{DD} \\
 V_M &= f(R_n, R_p)
 \end{aligned}$$

EE141

CMOS Inverter: Transient Response

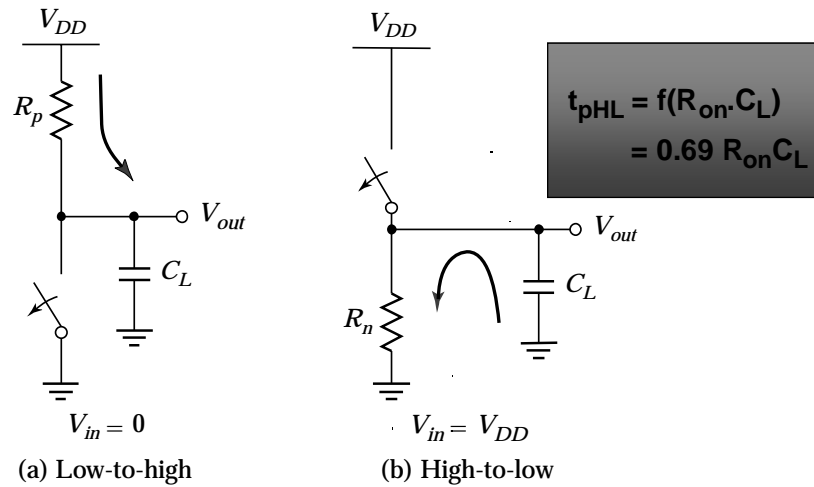


EE141

CMOS Properties

- Full rail-to-rail swing
- Symmetrical VTC
- Propagation delay function of load capacitance and resistance of transistors
- No static power dissipation
- Direct path current during switching


EE141

The MOS Transistor

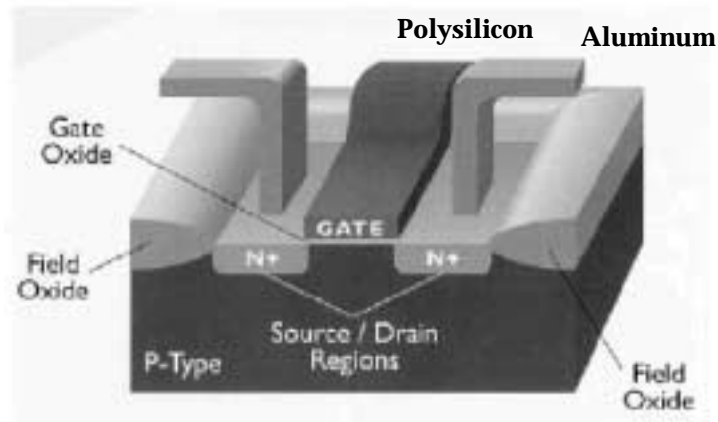


EE141


MOS Transistors - Types and Symbols

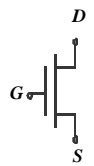


NMOS Enhancement

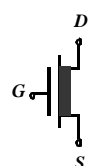

NMOS Depletion

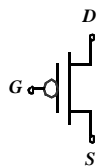


PMOS Enhancement

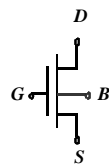

NMOS with
Bulk Contact

EE141

Threshold Voltage: Concept

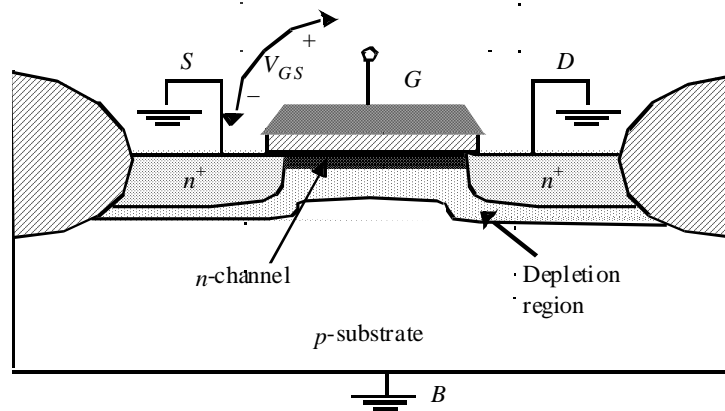

EE141

The Threshold Voltage

Threshold
$$V_T = V_{T0} + \gamma(\sqrt{|2\phi_F + V_{SB}|} - \sqrt{|2\phi_F|})$$

Fermi potential
$$\phi_F = \phi_T \ln\left(\frac{N_A}{n_i}\right)$$


$2\phi_F$ is approximately -0.6V for p-type substrates

γ - the body factor

V_{T0} is approximately 0.45V for our process

EE141

The Body Effect

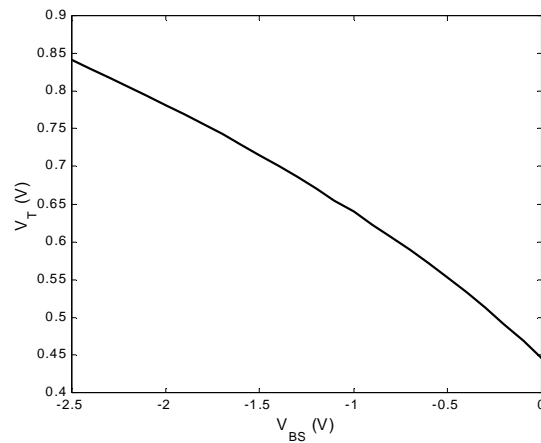

EE141

The Drain Current

Charge in the channel is controlled by the gate voltage:

$$Q_i(x) = -C_{ox}[V_{GS} - V(x) - V_T] \quad C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$$

Drain current is proportional to charge and velocity:

$$I_D = -v_n(x)Q_i(x)W$$

$$v_n = -\mu_n \xi(x) = \mu_n \frac{dV}{dx}$$

EE141

The Drain Current

Combining velocity and charge:

$$I_D dx = \mu_n C_{ox} W (V_{GS} - V - V_T) dV$$

Integrating over the channel:


$$I_D = k_n \frac{W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right] = k_n \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

Transconductance: $k_n' = \mu_n C_{ox} = \frac{\mu_n \epsilon_{ox}}{t_{ox}}$

EE141

Transistor in Linear


Linear (Resistive) mode

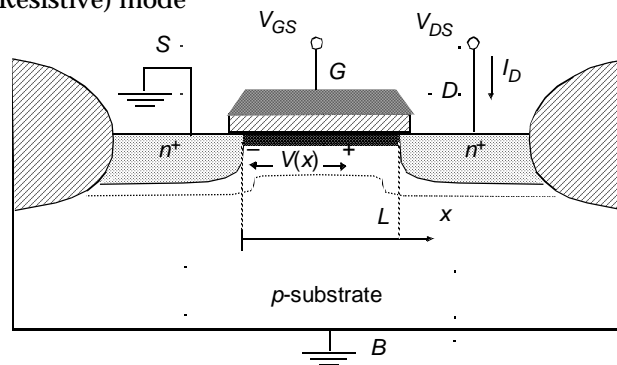

MOS transistor and its bias conditions

EE141

Transistor in Saturation

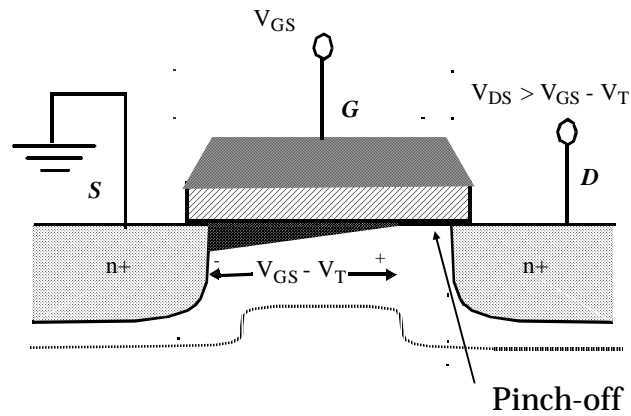

EE141

Saturation

For $V_{GD} < V_T$, the drain current saturates

$$I_D = \frac{k'_n W}{2 L} (V_{GS} - V_T)^2$$

Including channel-length modulation

$$I_D = \frac{k'_n W}{2 L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

EE141

Modes of Operation

Cutoff:

$$V_{GS} < V_T$$

$$I_D = 0$$

Resistive:

$$V_T < V_{GS}; V_{GS} - V_T > V_{DS}$$

$$I_D = \frac{k'_n W}{2 L} \left[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2} \right]$$


Saturation:

$$V_T < V_{GS}; V_{GS} - V_T < V_{DS}$$

$$I_D = \frac{k'_n W}{2 L} (V_{GS} - V_T)^2$$


EE141

Current-Voltage Relations A Good Ol' Transistor

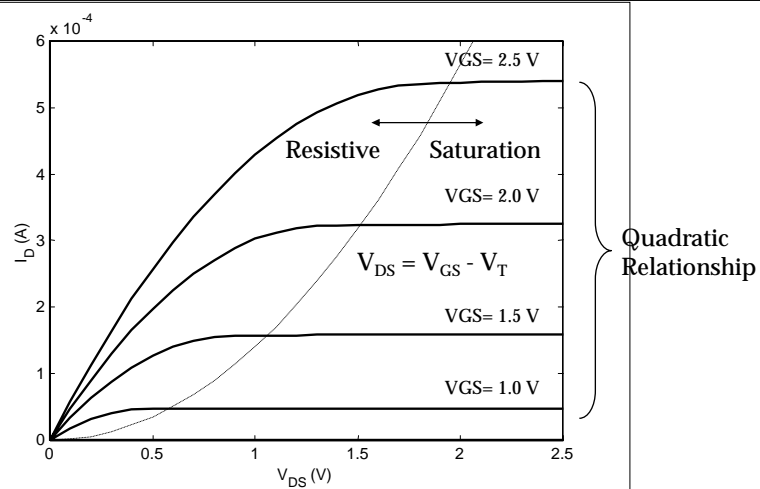

EE141

A model for manual analysis

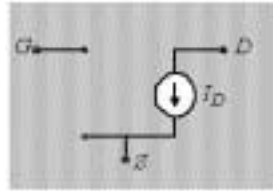

$$V_{DS} > V_{GS} - V_T$$

$$I_D = \frac{k_n W}{2 L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

$$V_{DS} < V_{GS} - V_T$$


$$I_D = k_n \frac{W}{L} \left((V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right)$$

with

$$V_T = V_{T0} + \gamma \left(\sqrt{|-2\phi_F + V_{SB}|} - \sqrt{|-2\phi_F|} \right)$$


EE141

Current-Voltage Relations The Deep-Submicron Era

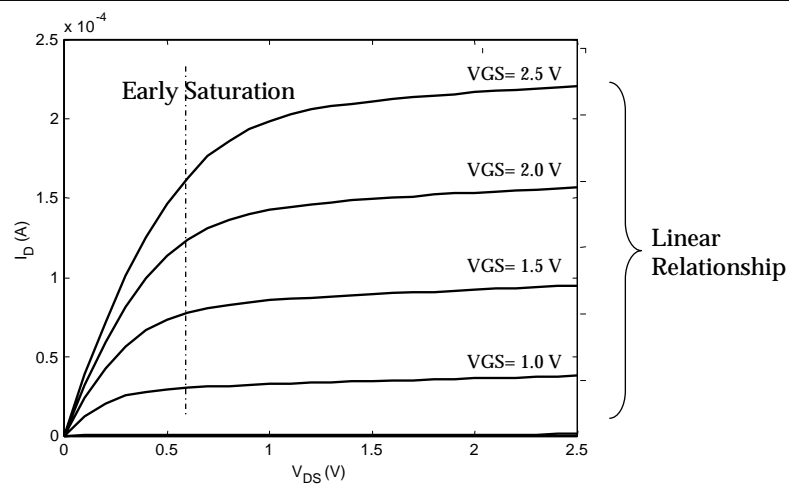


EE141

Velocity Saturation

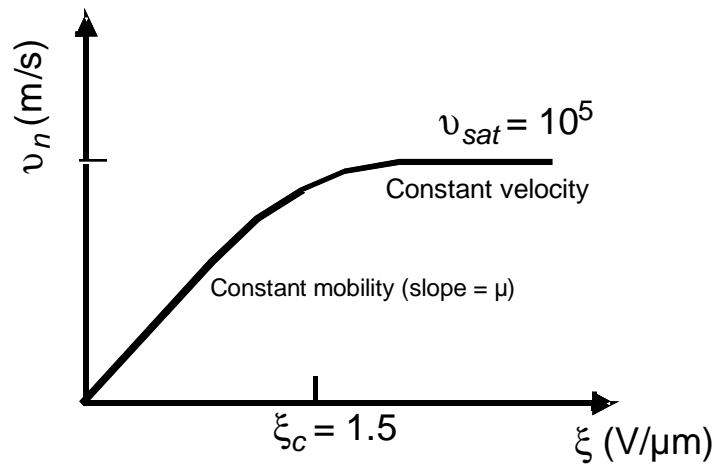


EE141

Velocity Saturation

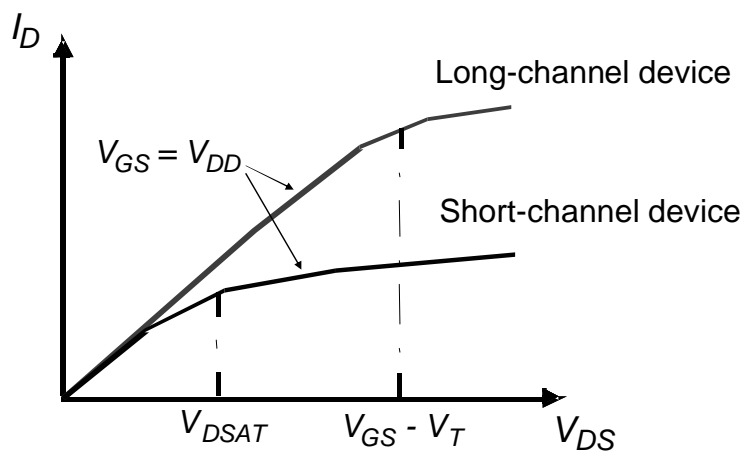


EE141

I_D versus V_{GS}

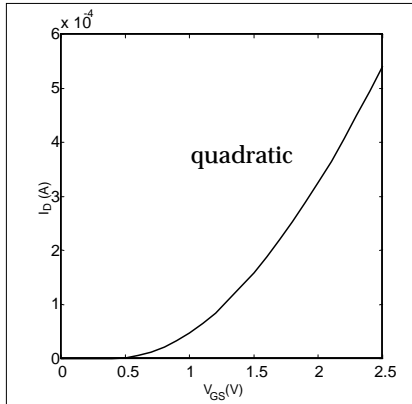


Long Channel

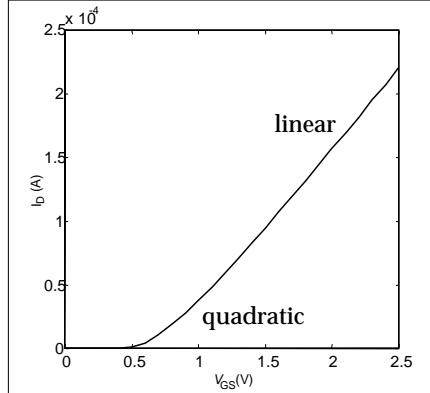


Short Channel

EE141

I_D versus V_{DS}

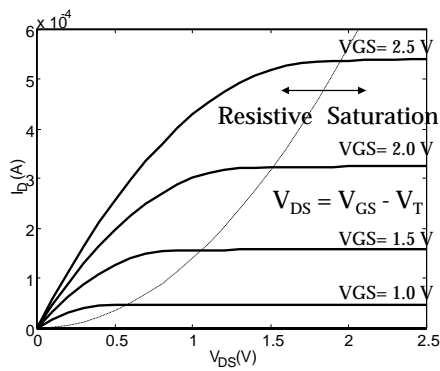

Long Channel

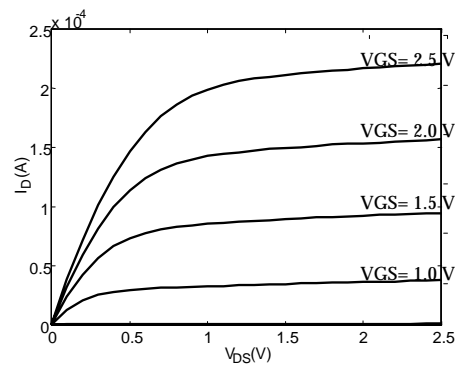

Short Channel

EE141

Including Velocity Saturation

Approximate velocity:

$$v = \frac{\mu_n \xi}{1 + \xi/\xi_c} \quad \text{for } \xi \leq \xi_c$$

$$= v_{sat} \quad \text{for } \xi \geq \xi_c$$


And integrate current again:

$$I_D = \frac{\mu_n C_{ox}}{1 + (V_{DS}/\xi_c L)} \left(\frac{W}{L}\right) \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$


In deep submicron, there are four regions of operation:
 (1) cutoff, (2) resistive, (3) saturation and (4) velocity saturation

EE141

Regions of Operation

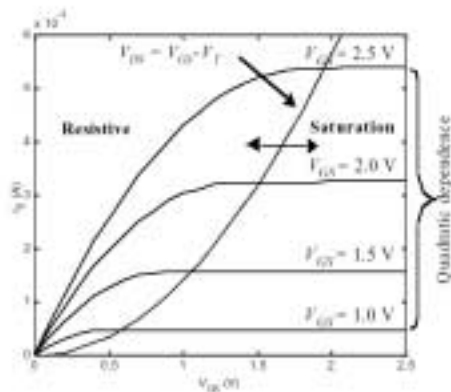


Long Channel

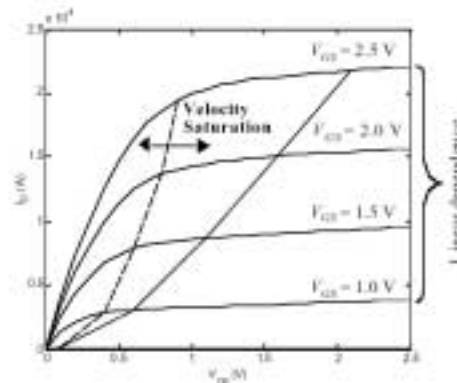

Short Channel

EE141

An Unified Model for Manual Analysis

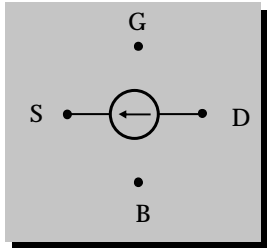

$$I_D = 0 \text{ for } V_{GT} \leq 0$$

$$I_D = k' \frac{W}{L} \left(V_{GT} V_{min} - \frac{V_{min}^2}{2} \right) (1 + \lambda V_{DS}) \text{ for } V_{GT} \geq 0$$


$$\text{with } V_{min} = \min(V_{GT}, V_{DS}, V_{DSAT}),$$

$$V_{GT} = V_{GS} - V_T,$$

$$\text{and } V_T = V_{T0} + \gamma (\sqrt{|-2\phi_F + V_{SB}|} - \sqrt{|-2\phi_F|})$$


EE141

Regions of Operation

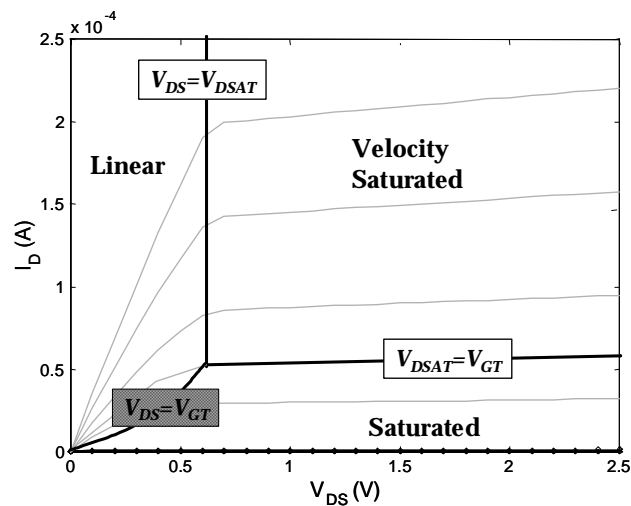

EE141

A PMOS Transistor

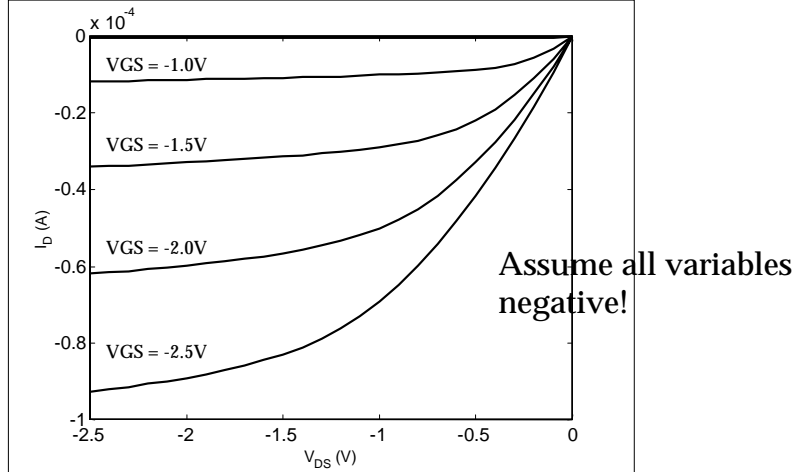

EE141


Transistor Model for Manual Analysis

Table 3.2 Parameters for manual model of generic 0.25 μm CMOS process (minimum length device).

	V_{T0} (V)	γ ($\text{V}^{0.5}$)	V_{DSAT} (V)	k' (A/V^2)	λ (V^{-1})
NMOS	0.43	0.4	0.63	115×10^{-6}	0.06
PMOS	-0.4	-0.4	-1	-30×10^{-6}	-0.1

EE141


The Transistor as a Switch

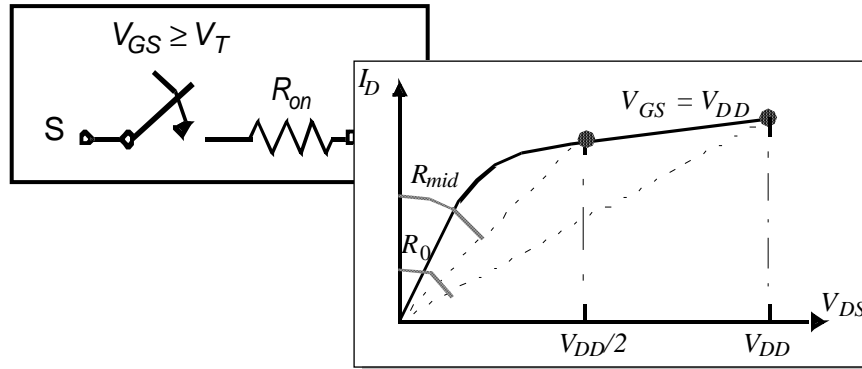

$$R_{eq} = \frac{1}{2} \left(\frac{V_{DD}}{I_{DSAT}(1 + \lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT}(1 + \lambda V_{DD}/2)} \right) \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{5}{6} \lambda V_{DD} \right)$$

EE141

The Transistor as a Switch

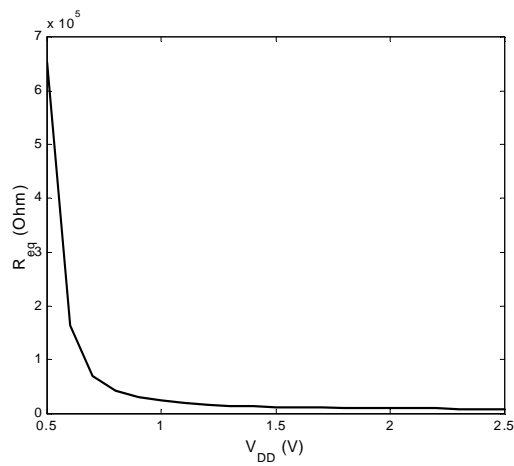

EE141


The Transistor as a Switch

Table 3.3 Equivalent resistance R_{eq} ($W/L = 1$) of NMOS and PMOS transistors in 0.25 μm CMOS process (with $L = L_{min}$). For larger devices, divide R_{eq} by W/L .

V_{DD} (V)	1	1.5	2	2.5
NMOS (k Ω)	35	19	15	13
PMOS (k Ω)	115	55	38	31

EE141

Future Perspectives

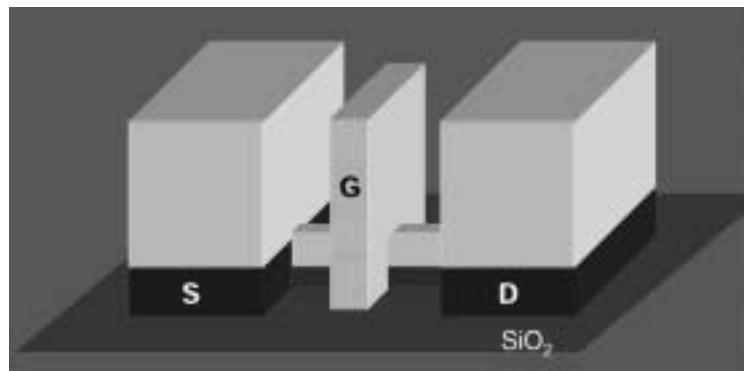

25 nm MOS transistor (Folded Channel)

EE141